

Power Electronic Technologies for Fuel Cell Power Systems

Presentation at
SECA 6th Annual Workshop
Pacific Grove, California
April 19, 2005

Dr. Jih-Sheng (Jason) Lai
Director, Future Energy Electronics Center
Virginia Polytechnic Institute and State University
Blacksburg, VA 24061-0111
TEL: 540-231-4741
FAX: 540-231-3362
Email: laijs@vt.edu

1

Outline

1. Basic Fuel Cell Power Systems
2. Non-isolated DC-DC Converters
3. Isolated DC-DC Converters
4. DC-DC Converter Implementation Issues
5. Basic DC-AC Inverters
6. Fuel Cell and Converter Interactions
7. Fuel Cell Energy Management Issues
8. Advanced V6 DC-DC Converter
9. Fuel Cell Current Ripple Issues
10. Recap

2

1. Basic Fuel Cell Power Systems

1. Fuel Cell Control

Flow rate
Pressure
Humidity
Temperature

BOP **Power Electronics**

Fuel in

Membrane
Electrode
Assembly
(MEA)

Core of fuel cell

2. Power Conversions


DC-DC for portable
DC-AC for household
DC-variable frequency
AC for automotive

Electricity
out

3. Energy storage


3

Automotive Fuel Cell Power System

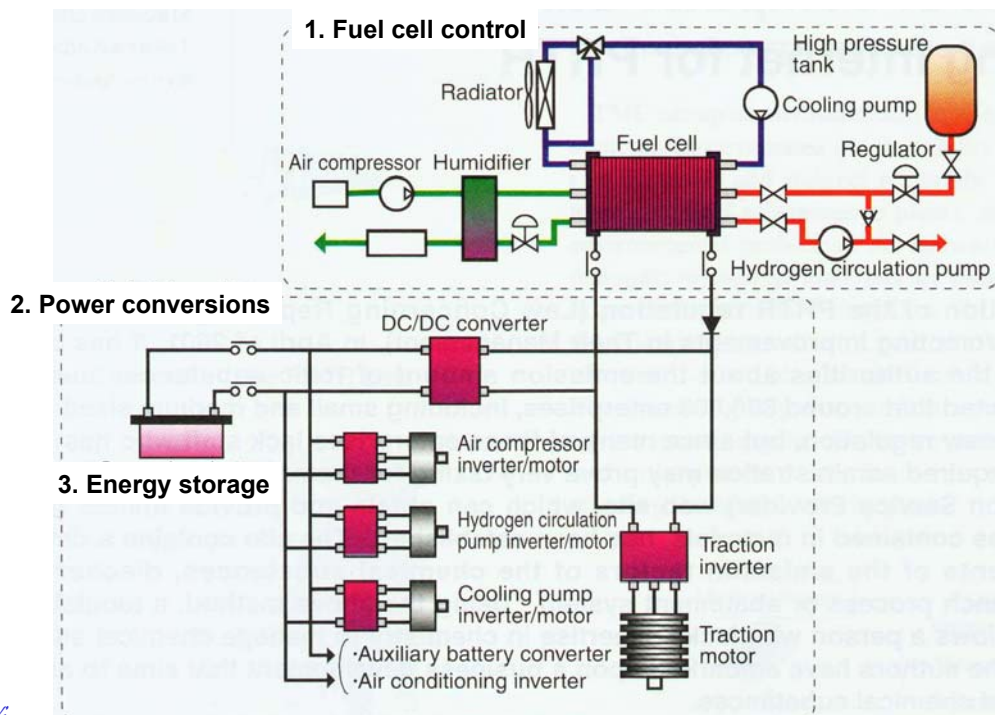

4

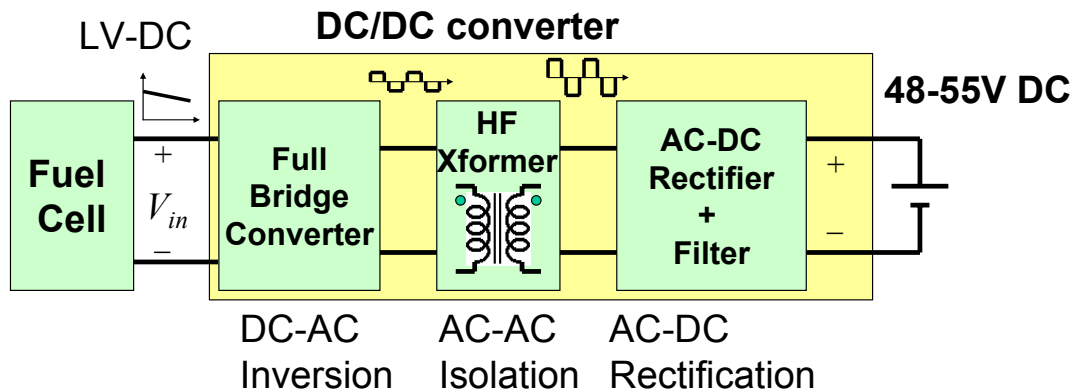
Stationary Fuel Cell Power Plant for Telecom Applications



- Fuel cell output or converter input is low-voltage DC with a wide-range variation
- Plant output is 48-V DC
- Isolation may or may not be needed

5

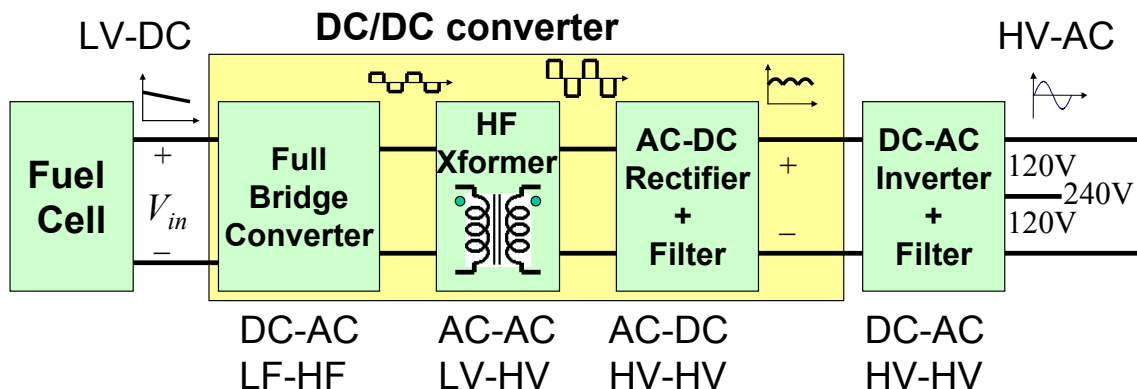Stationary Fuel Cell Power Plant for Household Applications



- Plant output is high-voltage ac
- Multiple-stage power conversions including isolation are needed

6



Major Issues Associated with the Power Conditioning Systems

- **Cost**
- **Efficiency**
- **Reliability**
- **Isolation**
- **Fuel cell ripple current**
- **Transient response along with auxiliary energy storage requirement**
- **Communication with fuel cell controller**
- **Electromagnetic interference (EMI) emission**

2. Basic Non-Isolated DC-DC Converters

- **Buck Converter – Output voltage is always lower than input voltage**
- **Boost Converter – Output voltage is always higher than input voltage**
- **Buck-boost Converter – Output voltage can be either lower or higher than input voltage**

Basic Principle of Buck Converter

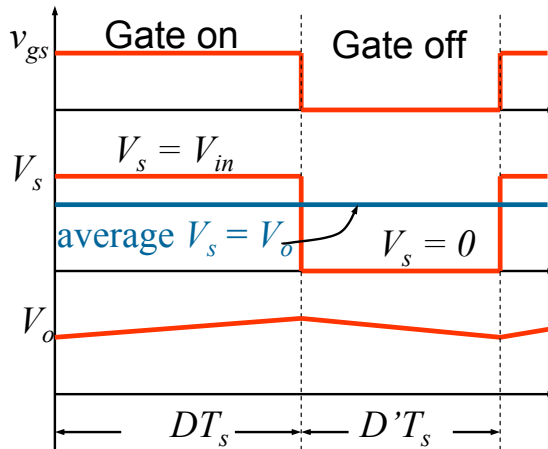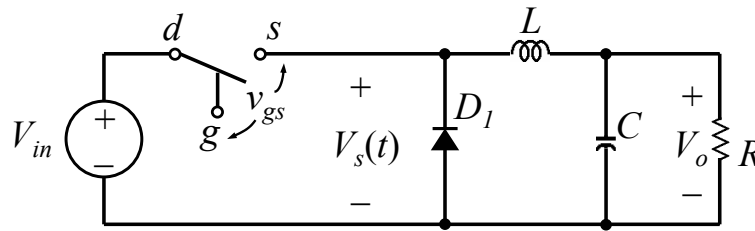

Average output voltage:


$$V_o = DV_{in}$$

where D is the duty ratio.
Because $D < 1$, V_o is always less than $V_{in} \rightarrow$ buck converting

T_s : switching period = $1/f_s$ (s)
 f_s : switching frequency (Hz)

9



A Buck Converter Example

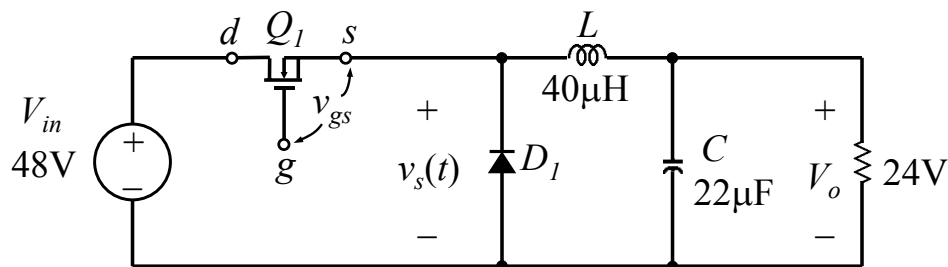

- Input is 48 V, and output is 24 V
- Duty cycle $D = V_o/V_{in} = 0.5$
- Switching frequency = 100 kHz
- Output power = 150 W
- Inductor and capacitor are designed to limit the current and voltage ripples

10

Basic Principle of Boost Converter

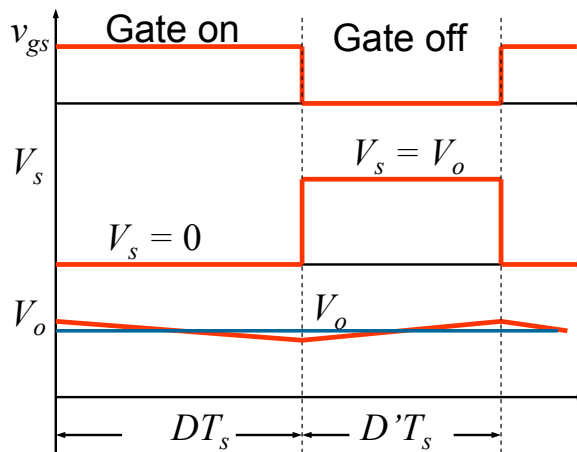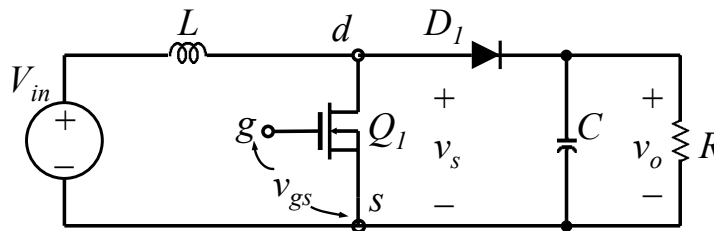


Average output voltage:

$$V_o = \frac{1}{1-D} V_{in} = \frac{1}{D'} V_{in}$$

where D is the duty ratio, and $D' = 1 - D$. Because $D' < 1$, V_o is always greater than $V_{in} \rightarrow$ boost converting

11



A Boost Converter Design Example

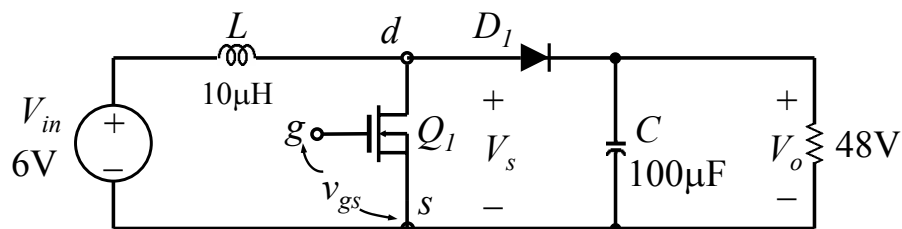

- Input is 6 V, and output is 48 V
- Duty cycle $D = 1 - V_{in}/V_o = 0.875$
- Switching frequency = 100 kHz
- Output power = 180W
- Inductor and capacitor are designed to limit the current and voltage ripples

12

Circuit Diagram of Buck-boost converter

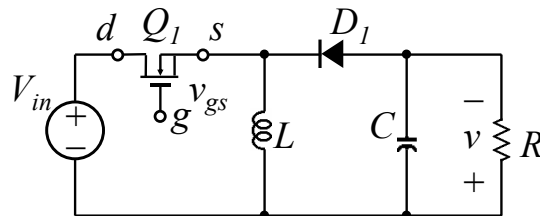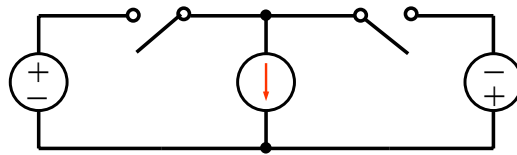


The output voltage can be expressed as

$$V = \frac{D}{1-D} V_{in} = \frac{D}{D'} V_{in}$$

13

Synchronous Rectifier

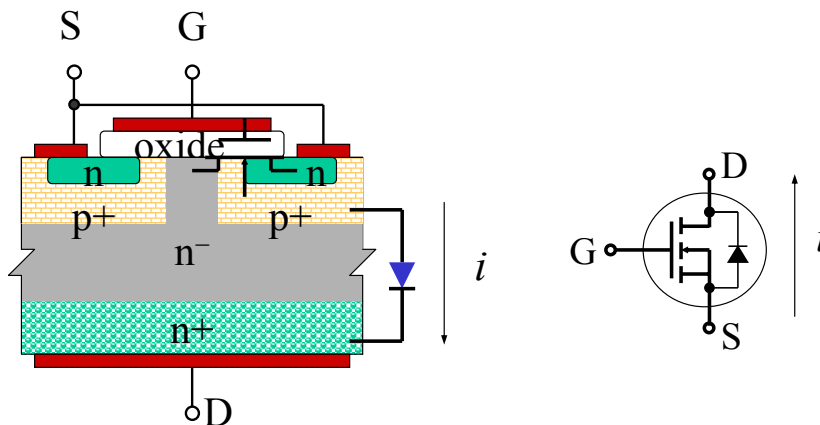

- MOSFET can be used as a diode by shorting G-S
- However, when running under diode mode, gating between G-S would allow current to flow through S-D channel in reverse direction → synchronous rectification



14

Features of Synchronous Rectification

- MOSFET voltage drop is resistive and can be as low as possible, such as <0.1 V.
- The voltage drop is very crucial to the converter efficiency in a low voltage system. For example, a diode with a fixed voltage drop of 0.7 V represents 3.5% loss of a 20-V system.
- Synchronous rectification allows the voltage drop to be a function of MOSFET resistance and current and cuts the conduction loss substantially. For example, a MOSFET with 5 m Ω running at 20 A condition, the voltage drop is 0.1 V, much less than diode voltage drop.
- Suitable for low-voltage systems.

15

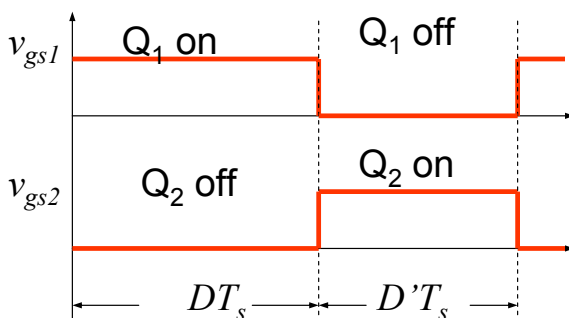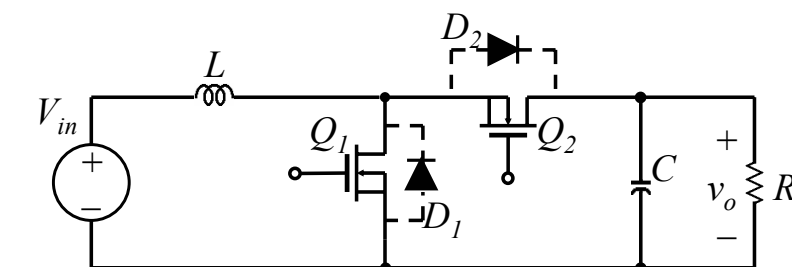
Circuit configuration of a Boost Converter with Synchronous Rectification



- D_1 and D_2 are body diode of Q_1 and Q_2 .
- Q_1 and Q_2 switch complimentary

16

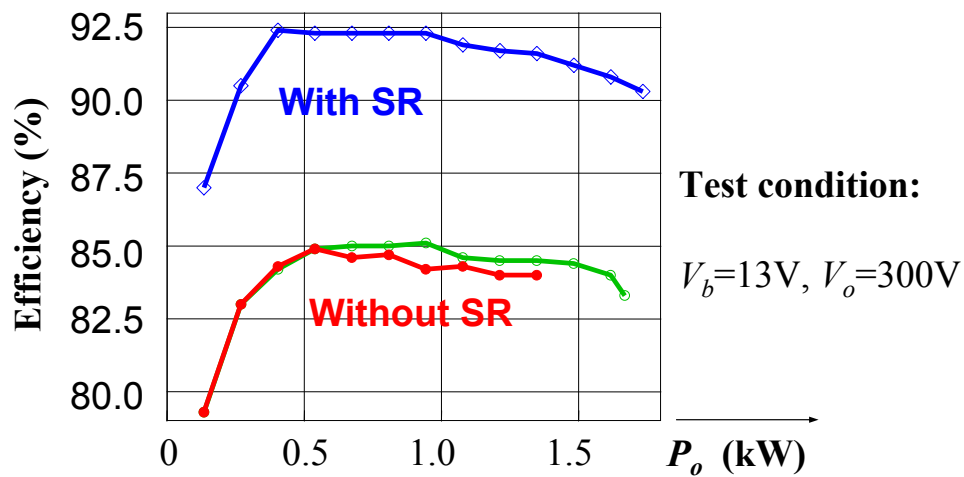Experimental Results of a DC-DC Converter with and without SR



Efficiency is improved by 7% with Synchronous Rectification

3. Isolated DC-DC Converters

- Why isolation is needed?
- Push-pull DC-DC converter
- Half-bridge DC-DC converter
- Full-bridge DC-DC converter


Isolation is Required for Most Systems

- **High voltage conversion ratios**
 - Isolation allows better device utilization
- **Grounding requirement**
 - Isolation avoids noise coupling
- **Safety requirement**
 - Isolation allows meeting safety standards
- **Multiple outputs**
 - Isolation transformer allows multiple secondary windings

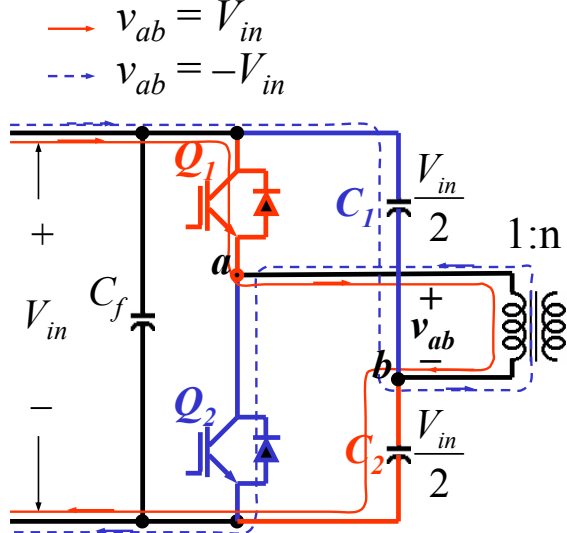
Problems with Isolation

- **Magnetic component design and cost are non-trivial**
- **Transformer saturation due to unbalance input**
- **Additional losses**
- **Additional terminations**

Basic Operating Principle of a Half-Bridge Converter Circuit





Half-bridge converter

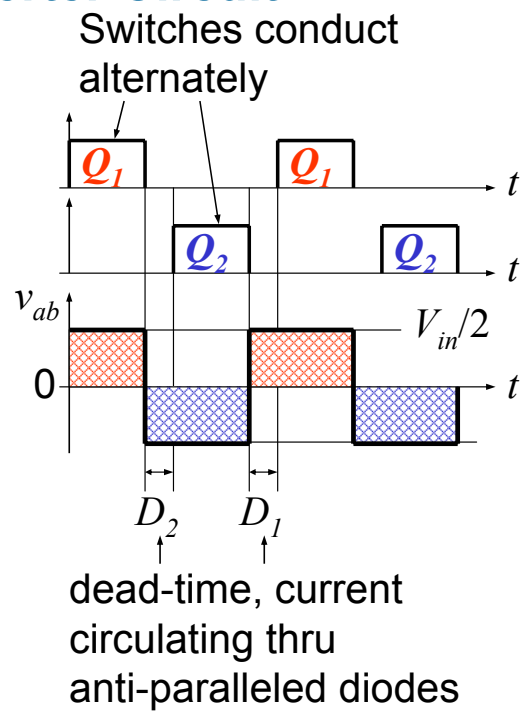

21



Half-Bridge DC/DC Converter

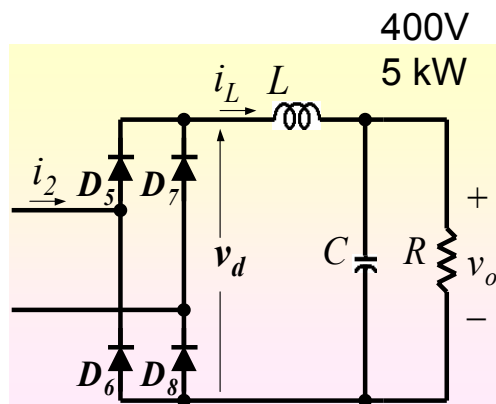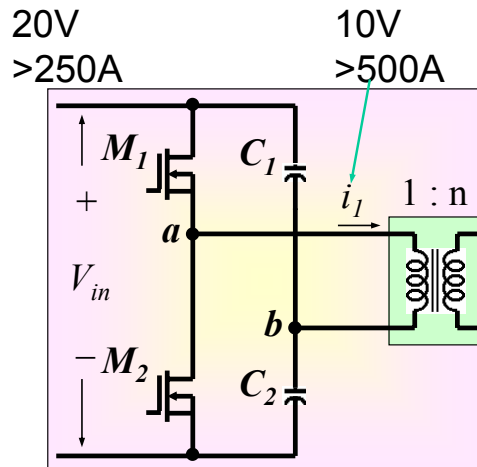

- ✓ Low device count
- ✓ Low voltage device
- ✗ Device sees twice current
- ✗ Unbalance due to split capacitors
- ✗ High leakage due to twice transformer turns ratio


22

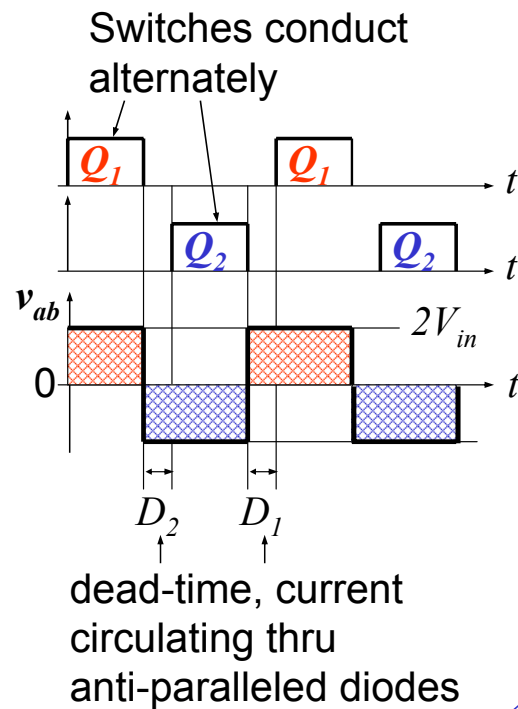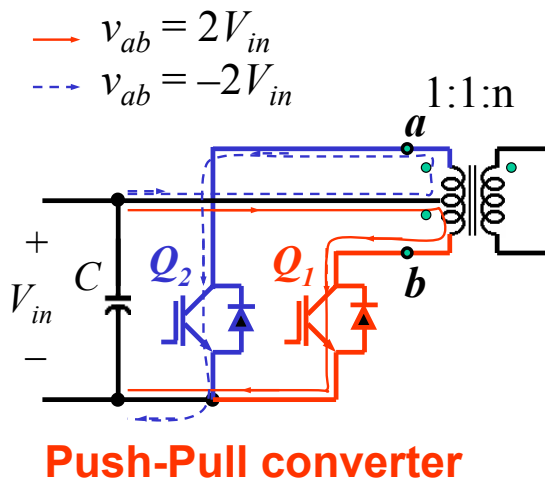Basic Operating Principle of a Push-Pull Converter




23

Push-Pull DC/DC Converter

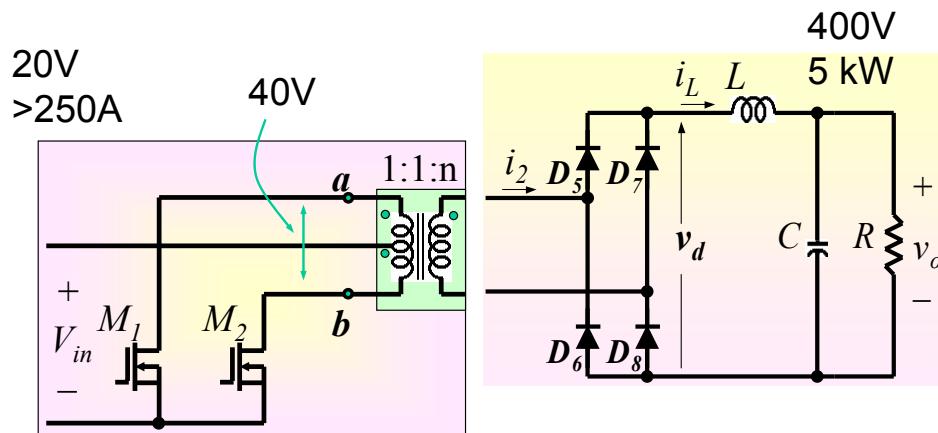

- + Simple non-isolated gate drives
- + Suitable for low-voltage low-power applications
- Device sees twice input voltage – need high voltage MOSFET
 - High conduction voltage drop, low efficiency
- Center-tapped transformer
 - Difficult to make low-voltage high-current terminations
 - Prone to volt-second unbalance (saturation)

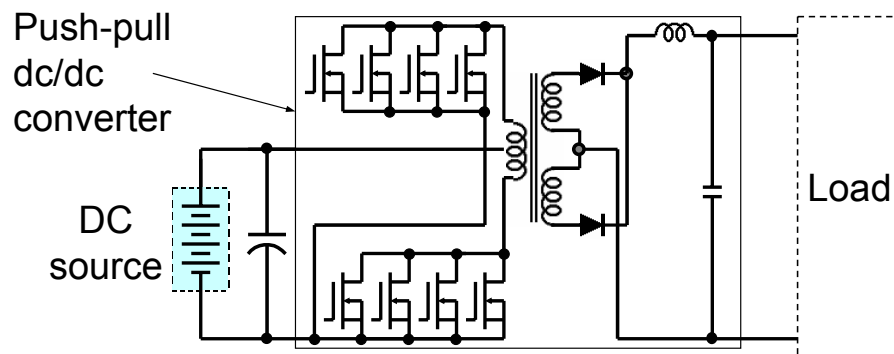
A Push-Pull Converter with Paralleled Devices



- Input – 28 to 35 V
- Device voltage blocking level – 100 V
- Efficiency – <85% even with 4 devices in parallel


25

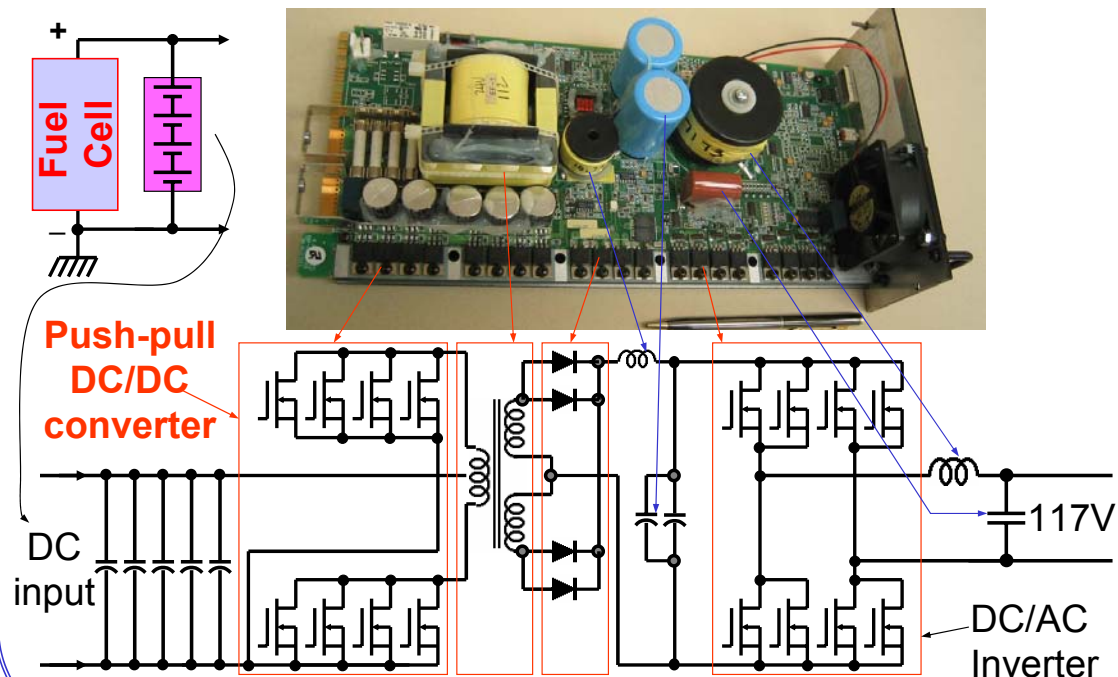A Commercial Off-the-Shelf 1-kW Fuel Cell Power Plant Using Push-Pull Converter




26

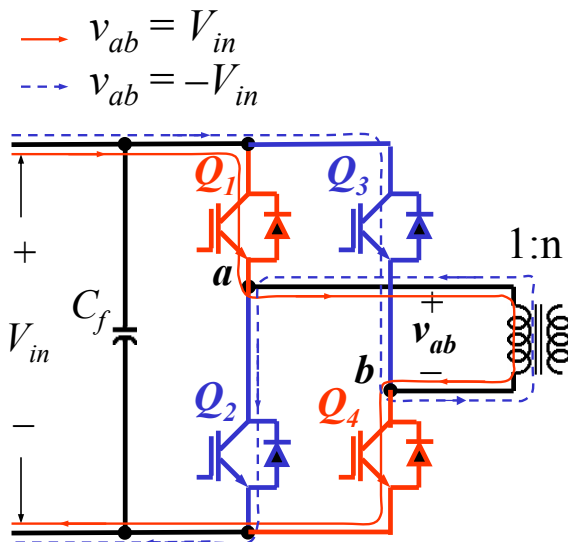Basic Operating Principle of a Full-Bridge Converter Circuit




Full-bridge converter

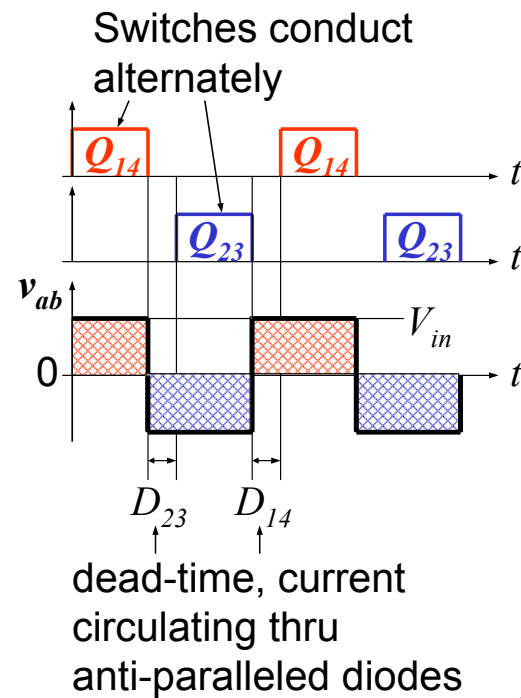

27


Full-Bridge DC/DC Converter

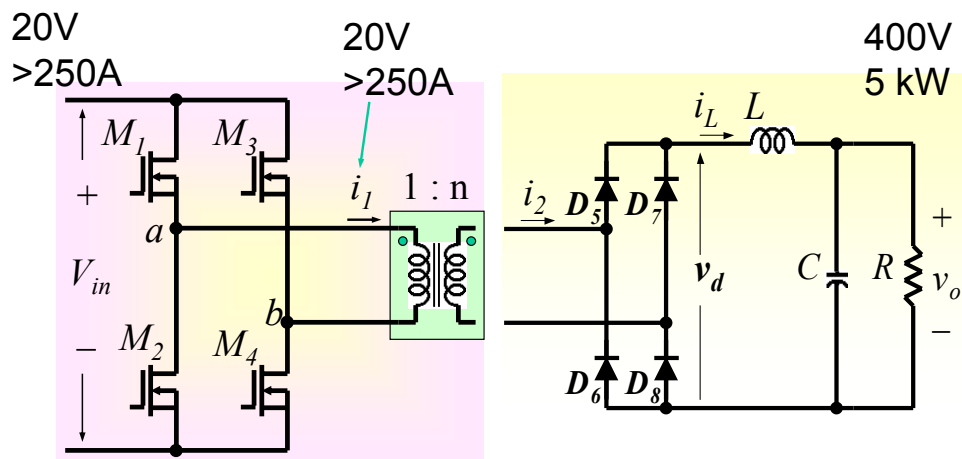

- ✓ Most popular circuit today for high-power applications
 - Soft switching possible
 - Reasonable device voltage ratings
- ✗ High component count from the look
- ✗ High conduction losses

28

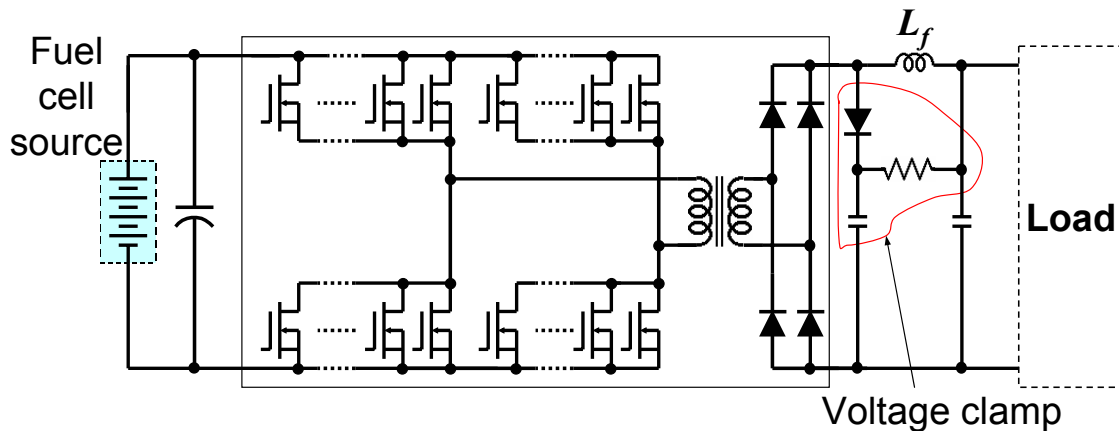Full-Bridge Converter with Paralleled Devices to Achieve Desired Power Levels



- Multiple devices in parallel to achieve desired high efficiency
- Problems are additional losses in **parasitic components, voltage clamp, interconnects, filter inductor, transformer, diodes**, etc.

29

Design Considerations for Isolated DC-DC Converters

- Transformer turns ratio
- Transformer core utilization
- Device voltage stress
- Device current stress
- Output diode voltage stress
- Voltage clamping

30

Pulse Width Modulation for Isolated DC-DC Converters

The average output voltage

$$V_o = DnV_{in}$$

Where

$$n = \text{transformer turns ratio} = n_2/n_1$$

$$D = \text{duty ratio} = t_{on}/T$$

and

n_1 = number of turns of primary winding

n_2 = number of turns of secondary winding

t_{on} = switch turn-on time

T = switching period

Transformer Core Utilization



× Forward: <50%

× Flyback: <50%

✓ Half-bridge: 100%

✓ Push-pull: 100%

✓ Full-bridge: 100%

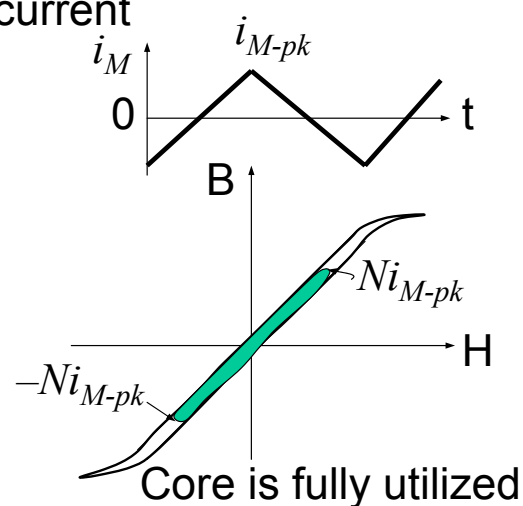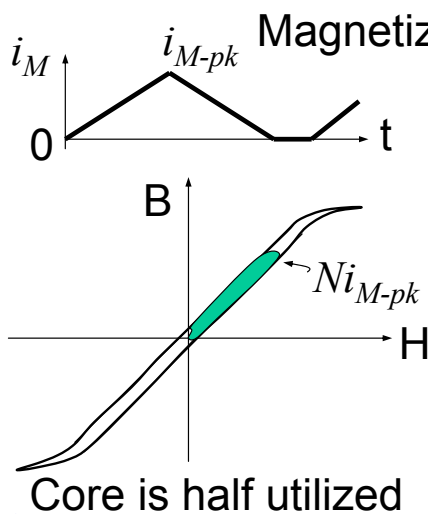

Device Voltage and Current Stresses

- **Device voltage stress**
 - × Push-pull: 200%
 - ✓ Half-bridge: 100%
 - ✓ Full-bridge: 100%
- **Device current stress**
 - × Half-bridge: 200%
 - ✓ Push-pull: 100%
 - ✓ Full-bridge: 100%
- **Output diode voltage stress**
 - × Center tap: 200%
 - ✓ Bridge: 100%



33

Voltage Clamping

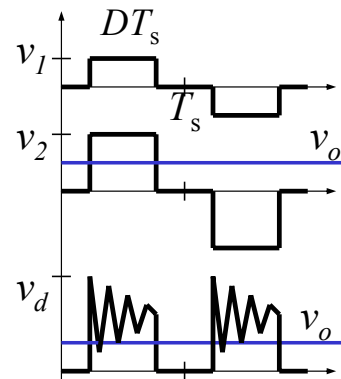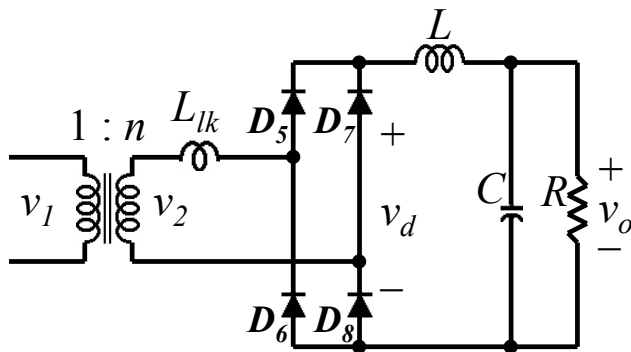- **Problems of diode over voltages**
 - Full-bridge
 - Center-tapped
- **Voltage clamping methods**
 - Passive clamping method
 - Active clamping method

34

Over-Voltage Caused by the Transformer Leakage Inductance





v_1 : Primary side voltage

v_2 : Secondary side voltage $v_2, v_2 > v_o$.

v_d : Voltage stress of upper diodes (D_5, D_7) when lower diodes (D_6, D_8) conduct, or vice versus, $v_{d-pk} > v_{2-pk} > v_o$, due to leakage inductance voltage drop.

35

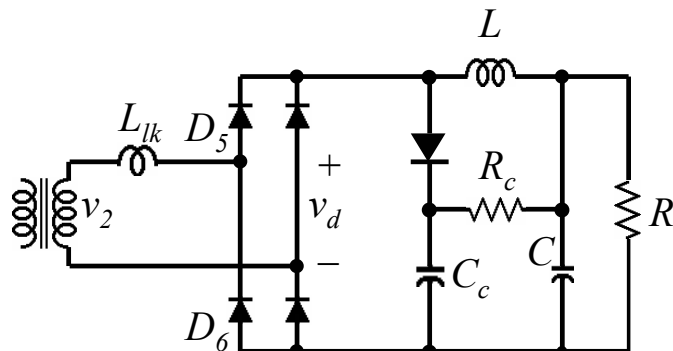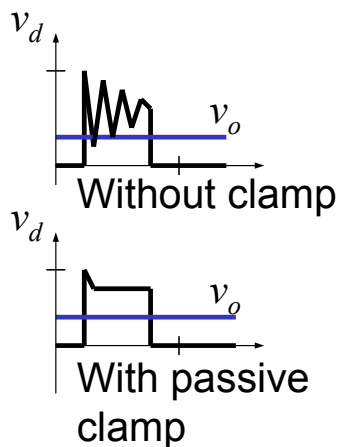Full-Bridge Diode Rectifier Over-Voltage Clamping



Advantage: Diode voltage stress is significantly reduced.

Disadvantage: Added cost and complexity.

36

Fuel Cell System Example for Topology Selection

Question: With 48 V fuel cell voltage and 400 V dc output, what topology is the best?

Answer: Intuitively, **push-pull converter** is the best because of least parts count. However, with device availability and cost consideration, **full-bridge converter** may be a better choice.

Reason: For low-side power MOSFET, lower voltage is more cost effective. Similarly, for high-side diode, lower voltage is more cost effective.

4. Implementation Issues in High Power DC/DC Converters


- **Controller output duty cycles tend to be unbalanced due to internal chip layout, resulting transformer saturation.**
- **Voltage sensing problem:**
 - Feedback voltage signal tends to be corrupted by noises
 - Hall sensor is expensive
 - Common mode and isolation are difficult to deal with resistor dividers
- **Current sensing problems:**
 - Lossy with resistor sensing
 - Difficult to insert Hall sensor for device current measurement

Full-bridge Converter Design Example

- **Specifications:**
 - Input fuel cell voltage ranges from 36 V to 60 V
 - Output: 400 V, 10 kW
- **Current**
 - Output: 25 A
 - Input: 208 A

39

Power Stage Design

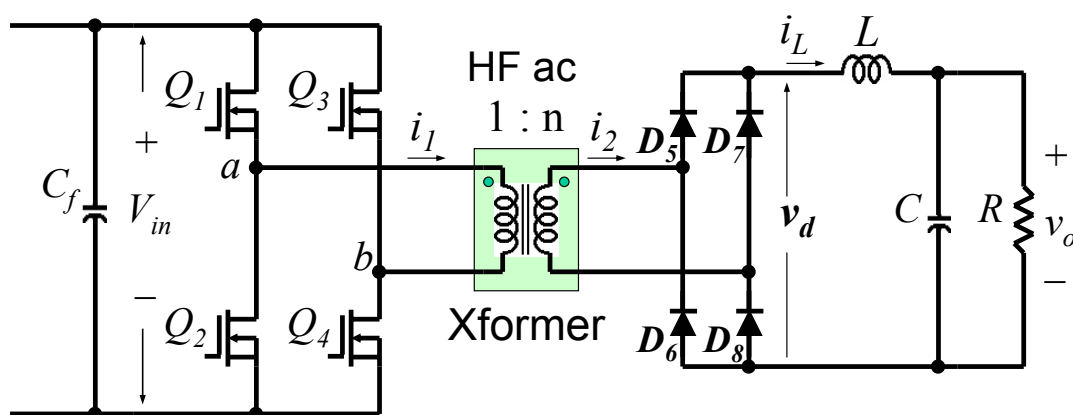

Component Design and Selection:

- Power MOSFET
- Rectifier diode
- Transformer
- Filter inductor
- Filter capacitor

40

Survey of High Current Power MOSFETs

| Manufacturer | Part Number | V_{DSS} (V) | R_{DS-on} (m Ω) | Package |
|-------------------------|---------------|---------------|---------------------------|-----------------|
| Fairchild | FDB045AN08A0 | 75 | 4.5 | TO-263 |
| International Rectifier | IRFP2907 | 75 | 4.5 | TO-247 |
| Fairchild | FDP047AN08A0 | 75 | 4.7 | TO-220AB |
| IXYS | FMM 150-0075P | 75 | 4.7 | ISOPLUS i4-PAC* |
| Vishay Siliconix | SUM110N08-05 | 75 | 4.8 | TO-263 |
| IXYS | IXUC160N075 | 75 | 6.5 | ISOPLUS 220 |
| International Rectifier | IRF3808 | 75 | 7.0 | TO-220AB |
| Fairchild | FQA160N08 | 80 | 7.0 | TO-3P |

| Quantity | 1 | 100 | 1000 | 25,000 | 50,000 | 100,000 |
|---------------|--------|--------|--------|--------|--------|---------|
| FDB045AN08A0 | \$3.50 | \$2.50 | \$2.40 | \$2.30 | \$2.10 | \$1.60 |
| IRFP2907 | \$4.49 | \$3.96 | \$3.07 | \$3.07 | \$3.07 | \$2.89 |
| FDP047AN08A0 | \$3.50 | \$2.50 | \$2.40 | \$2.30 | \$2.10 | \$1.60 |
| FMM 150-0075P | \$8.00 | \$7.00 | \$6.19 | \$5.79 | \$5.30 | \$5.03 |
| SUM110N08-05 | \$2.70 | \$2.50 | \$2.50 | \$2.35 | \$2.19 | \$2.19 |
| IXUC160N075 | \$4.00 | \$3.00 | \$2.05 | \$1.65 | \$1.49 | \$1.40 |
| IRF3808 | \$2.29 | \$2.16 | \$1.80 | \$1.50 | \$1.30 | \$1.17 |
| FQA160N08 | \$4.00 | \$3.00 | \$2.90 | \$2.60 | \$2.50 | \$2.20 |

*Note: IXYS FMM 150-0075 is a dual pack (half bridge) device.

41

Survey of Ultrafast Reverse Recovery Diodes

| Manufacturer | Part Number | V_F | t_{rr} | I | Package |
|-------------------------|-------------|-------|------------|------|----------|
| Fairchild | RHRG5060 | 1.5 V | 45ns (max) | 50 A | TO-247 |
| International Rectifier | HFA50PA60C | 1.9 V | 23ns (typ) | 50 A | TO-247AC |
| IXYS | DSEK 60-06A | 1.6 V | 35ns (typ) | 60 A | TO-247AD |

| Quantity | 1 | 100 | 1000 | 25,000 | 50,000 | 100,000 |
|-------------|---------------------|--------|--------|--------|--------|---------|
| RHRG5060 | N/A, (300 part min) | | \$3.50 | \$1.75 | \$1.50 | \$1.50 |
| HFA50PA60C | \$8.81 | \$8.22 | \$7.71 | \$7.61 | \$7.25 | \$4.00 |
| DSEK 60-06A | \$4.00 | \$3.00 | \$2.50 | \$2.07 | \$1.99 | \$1.90 |

42

Output Filter Capacitor Selection

- Typically based on the output voltage ripple


- The output filter capacitor needs to handle 120 Hz, 22 A ripple current generated from the next stage inverter.
- Assume the **voltage ripple** is limited to 5%. The capacitance can be calculated as

$$C = \frac{\Delta I}{8f \cdot \Delta V} = \frac{22}{8 \cdot 60 \cdot 400 \cdot 0.05} = 2.2 \text{ mF}$$

Digital Computer Implementation for High Power DC/DC Converters

- Digital computer such as DSP has become a good option for high power DC/DC converter control implementation
- Feedback voltage signal can be converted to digital and through PWM feeding back to DSP to avoid noise corruption
- Even if commercial PWM or PSM chips are used, the control signal can be obtained from DSP through D/A conversion
- Communication with digital signals has become the essential part between the dc/dc converter and the fuel cell controller or other power converters

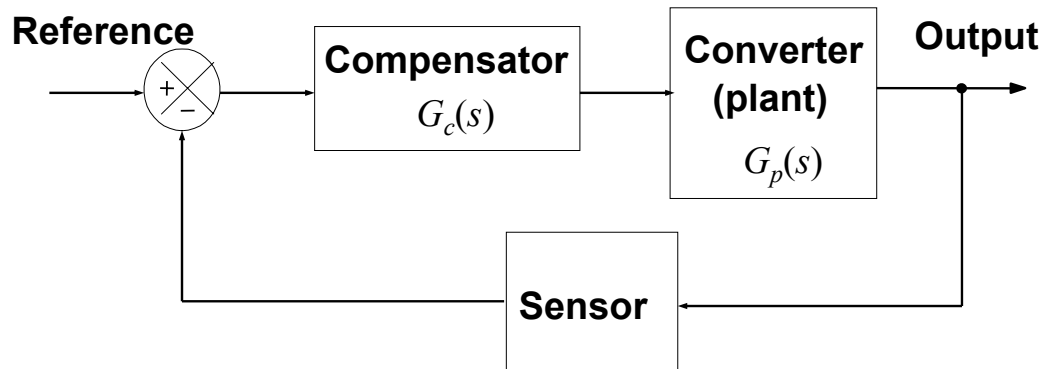Controller Design for a Typical Converter




$$G_p(s) = \frac{K}{1 + \frac{s}{Q} + s^2} \quad s = j\omega = 2\pi f \quad j = \sqrt{-1} \quad f = \text{frequency}$$

$$G_c(s) = K_p + \frac{K_i}{s} \quad (\text{A standard PI controller})$$

45

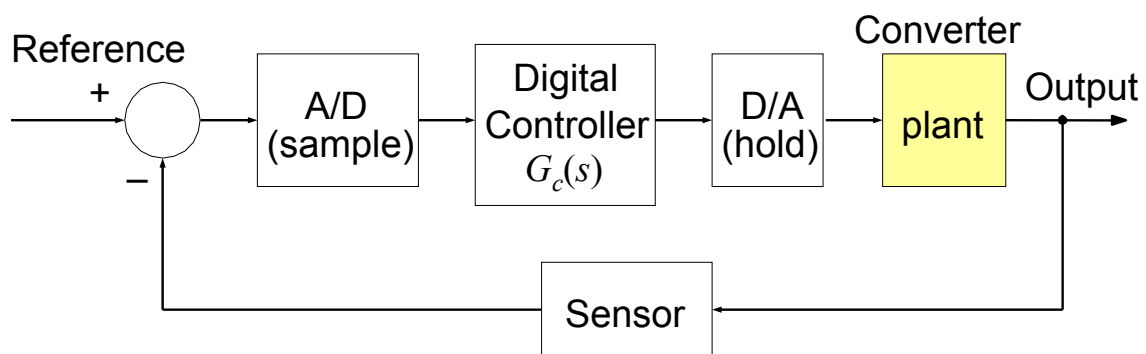Digital Controller for a Typical Converter




$$G_c(z) = K_p + K_i \frac{T_s}{2} \frac{z+1}{z-1}$$

T_s = switching frequency

$$s = \frac{2}{T_s} \frac{z-1}{z+1}$$

46

Voltage Loop Controller Block Diagram

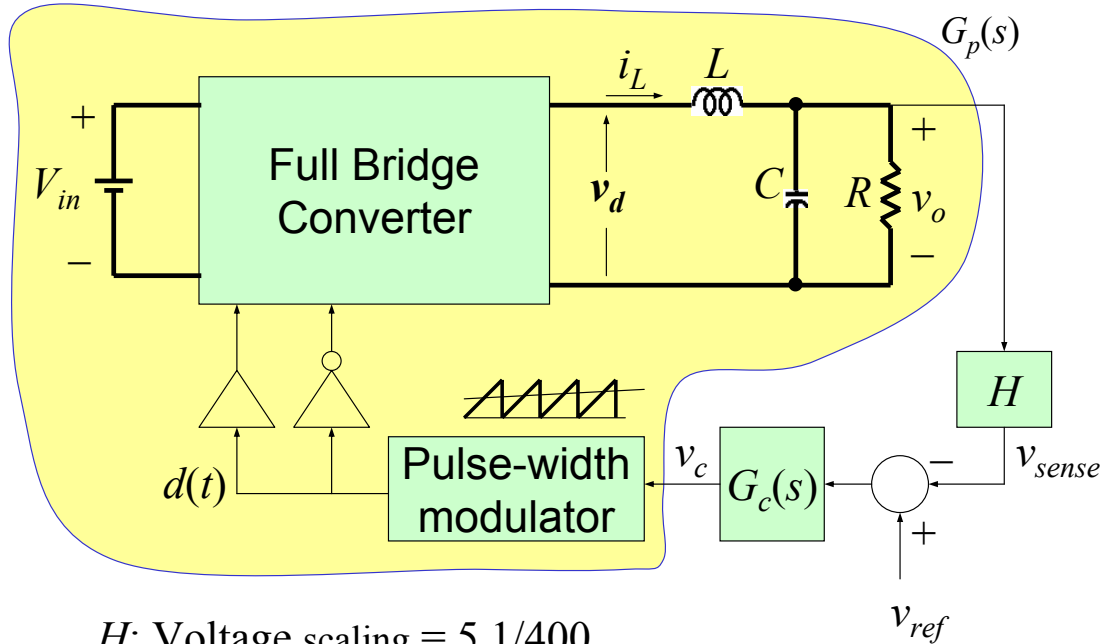


H : Voltage scaling = 5.1/400

$G_c(s)$: PI or PID Controller

47

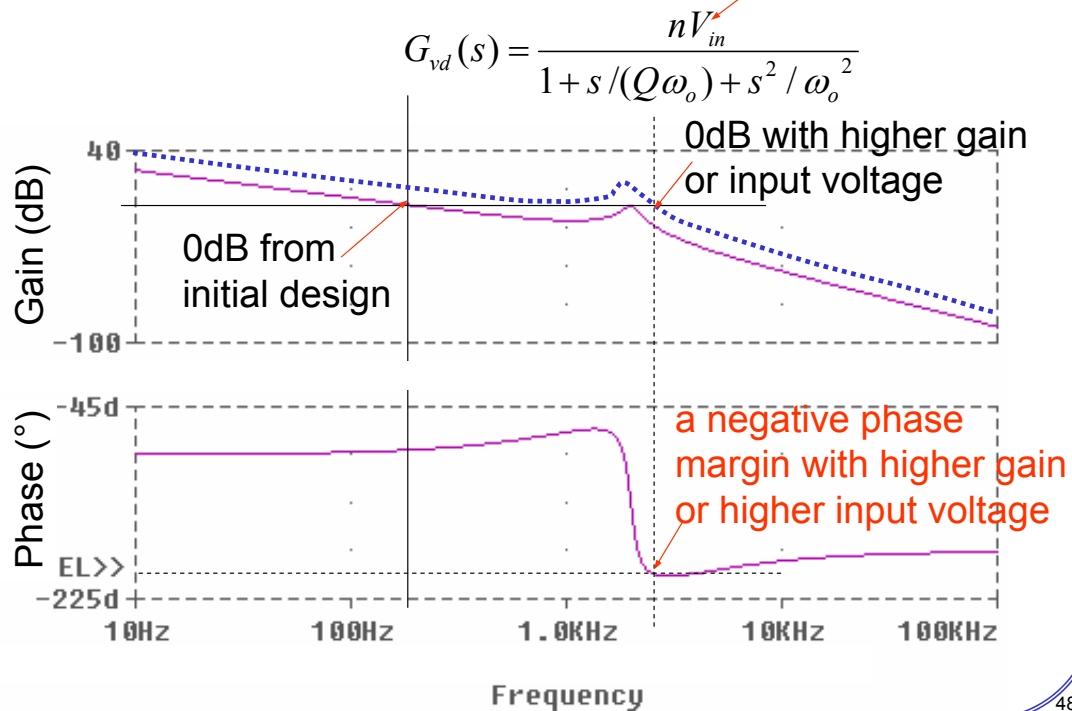Phase Margin Shifts due to Fuel Cell Input Voltage Variation: 42 to 60 V



48


DC-DC Converter Control System Design is Challenging with the Fuel Cell Source

- A typical controller is designed with **low input voltage** and **heavy load** condition.
- When the load is reduced, the fuel cell voltage increases, and the original controller design may be inadequate due to **input voltage variation**.
- Increasing the input voltage is equivalent to increase the closed-loop gain and tends to worsen the phase margin, and the system can eventually become **unstable**.

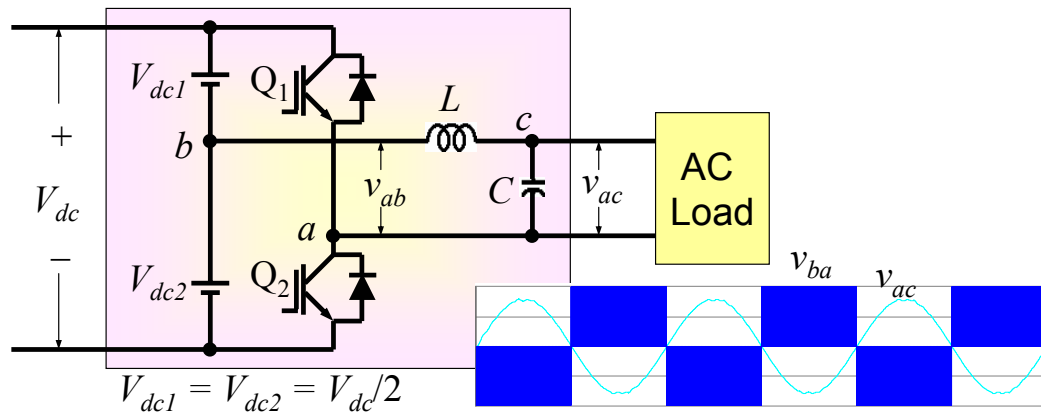5. DC/AC Inverters

- **Single-phase output**
 - Half-bridge
 - Full-bridge
- **Dual single-phase outputs**
 - Dual half-bridge
 - Three-leg inverter
- **Load Effect**
 - Linear loads
 - Nonlinear loads

Half-Bridge DC-AC Inverter with Split DC Buses




Maximum output peak voltage $V_{max} = V_{dc}/2$

- Simple dc-ac Inverter with **minimum switch counts**
- Split dc buses should be very **stiff and balance** to avoid dc or even harmonics at the ac output
- Control is limited to the ordinary sinusoidal pulse width modulation (**SPWM**)
- Cost burden is in **passive components**

51


Sinusoidal Pulse Width Modulation

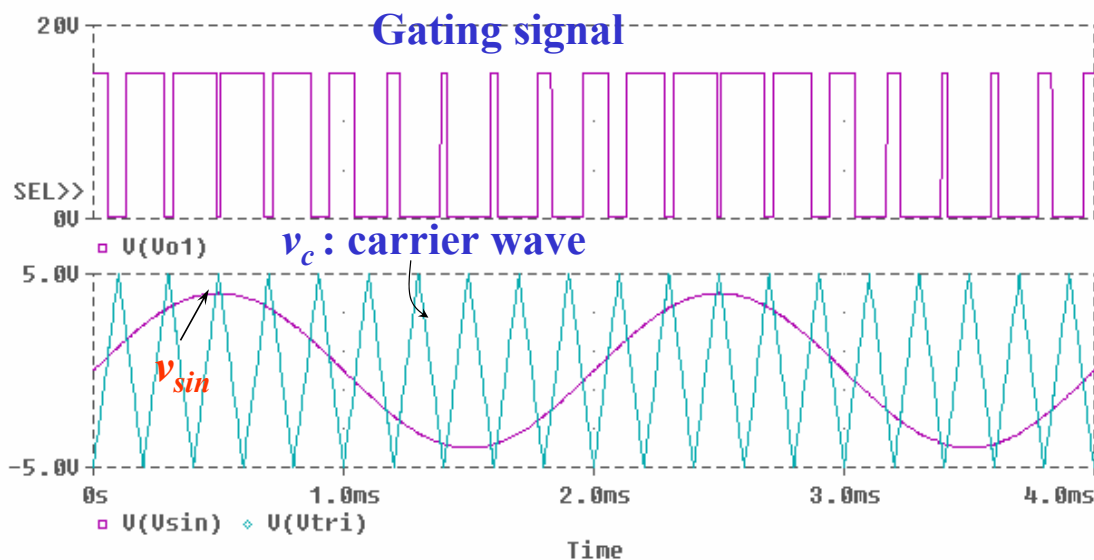

When $v_{sin} > v_c$, gate signal is high, and IGBT is turned on;
Otherwise, gate signal is low and IGBT is turned off.

52

Single-Phase Full-Bridge DC-AC Inverter

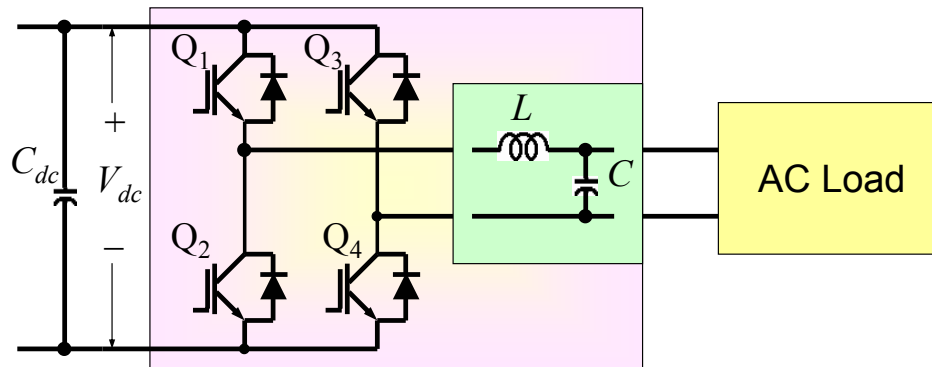


Compared with Half-Bridge inverter, FB inverter features

- Simple dc-ac Inverter with **more switch counts, but less bulky capacitors**
- Control is more flexible to have phase-shifted **SPWM** for two individual legs – Dual Modulation Method.
- Size of **passive components** may be reduced

53

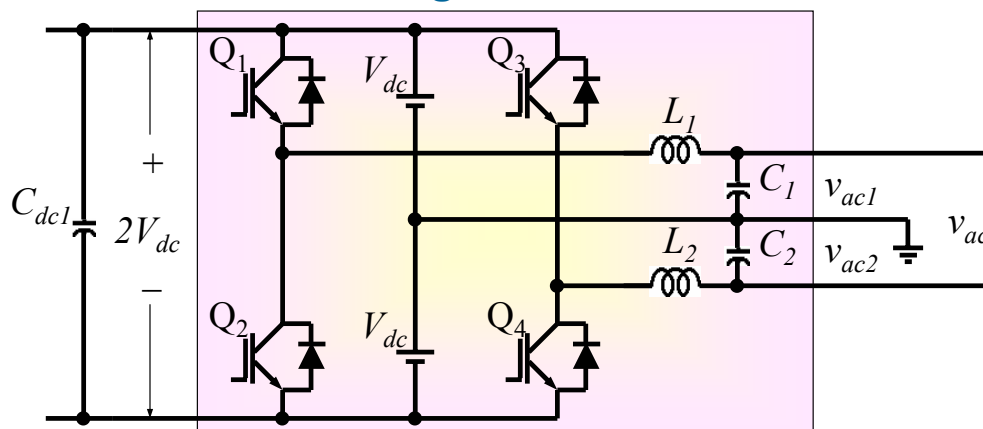
Dual Single-Phase Outputs with Dual Half-Bridge Inverters



- ✓ Only one set of split dc buses are required
- ✓ Q_1 - Q_2 and Q_3 - Q_4 pairs need to be switched complementary so that the total $v_{ac} = v_{ac1} + v_{ac2}$.
- ✗ Possible unbalanced output ac voltages under unbalanced load conditions

54

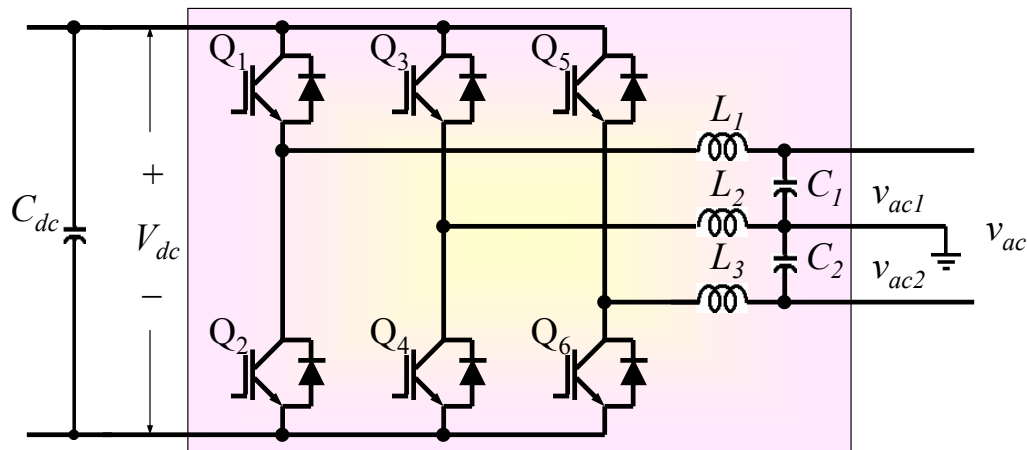
Three-leg Inverter for Dual AC Outputs with Single DC Bus



- Similar to full-bridge inverter with **more switch counts, but less bulky capacitors**
- Outer legs do SPWM to produce v_{ac} output. Middle leg is controlled to equalize v_{ac1} and v_{ac2}
- Control is more complicated to ensure output voltage balance
- Size of **passive components** may be reduced

55

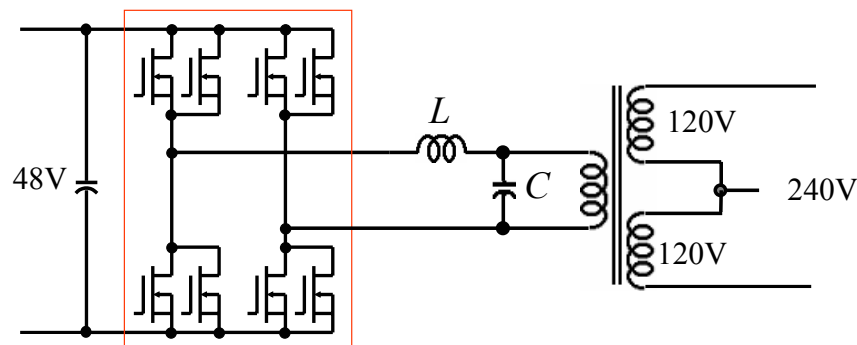Using Low-Frequency Transformer for Low-Voltage AC Inverter Output





Features:

- Low-frequency transformer allows low-voltage DC to be directly converted to AC
- Output can be single or dual
- Size is the major concern

56

Inverter Output with Resistive Load

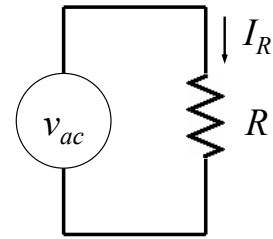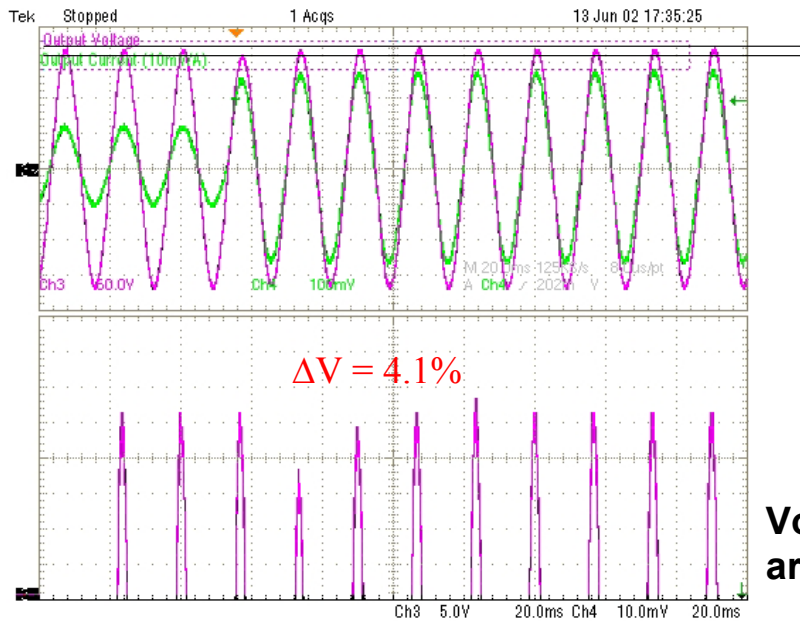


$$I_R = \frac{v_{ac}}{R}$$

Voltage and current are in phase


57

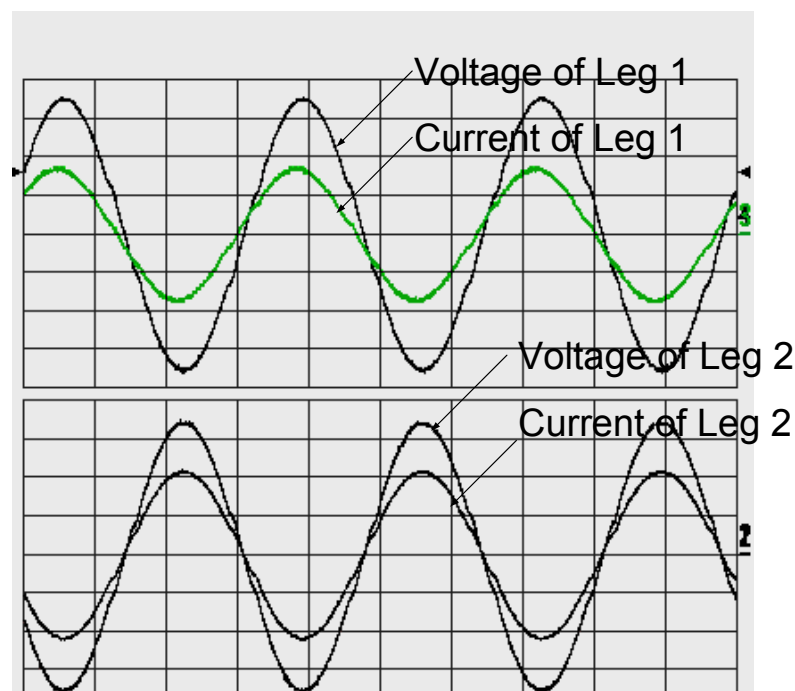Dual Output Voltage and Current with Unbalanced and Reactive Loads





58

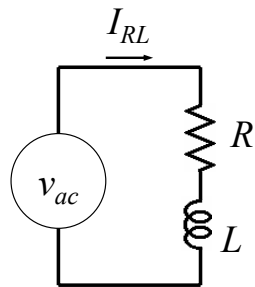Majority of Power System Loads is Inductive



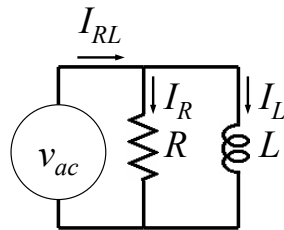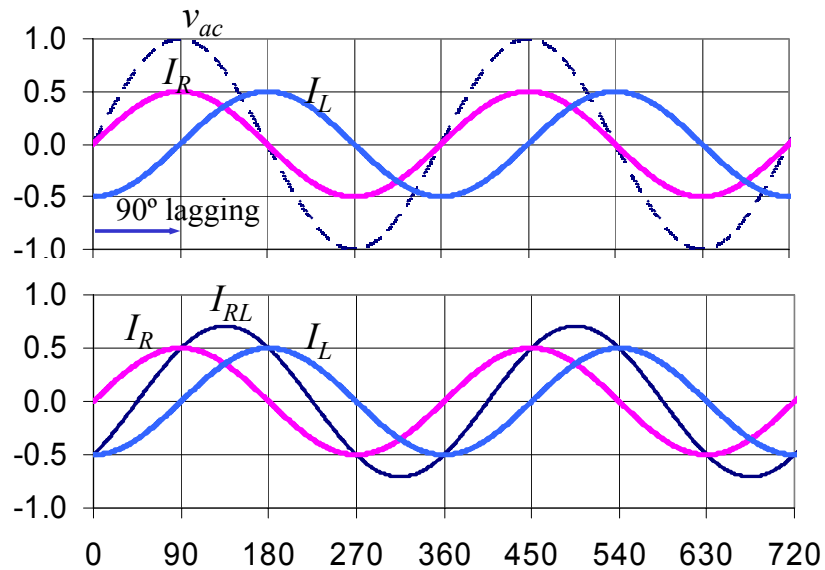
Impedance of inductor is imaginary (90° apart from real value)




$$X_L = j\omega L = j2\pi fL$$

59


What about Watt and VAR?

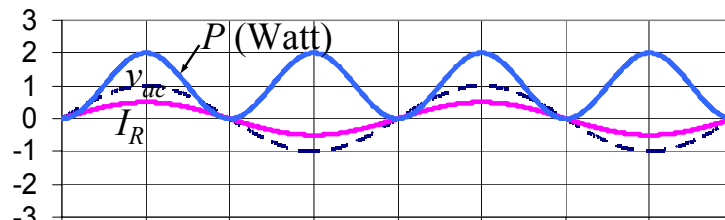

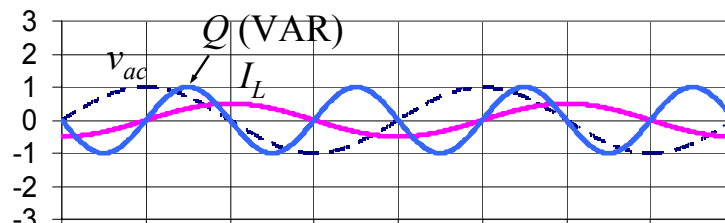Watt is **real** $V \times A$, average Watt > 0 , and is the average $(V \times A)$.



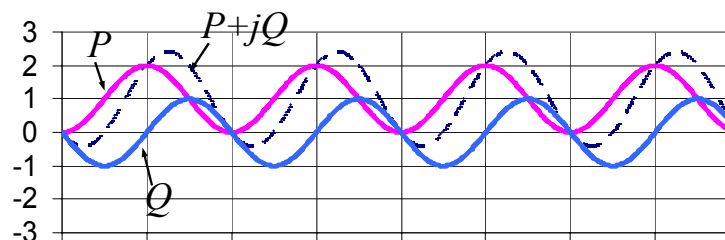VAR is **reactive** $V \times A$, average VAR = 0, but reactive current is not 0.



$VA = \text{Watt} + j\text{VAR}$, not Watt+VAR because they are not in phase.


60

Implications of VAR


- **Average VAR = 0 → No real power output**
- **VAR loads are typically inductive such as motors, magnetic ballasts, relays, etc.**
- **The current associated with VAR causes additional heat losses in the wiring and the internal impedance of the source**
- **Inductive VAR can be compensated with capacitive VAR, but not without complexity**
- **Nonlinear loads also introduce VAR**

61

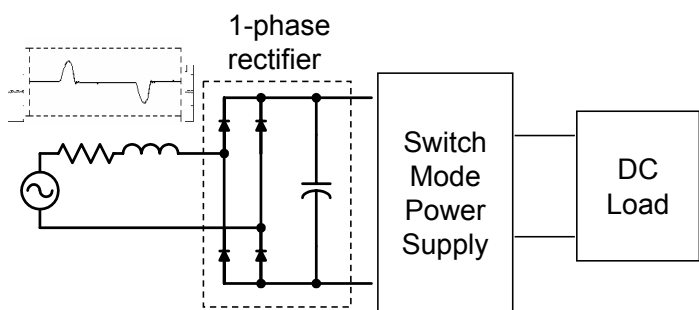Majority of Electronic Loads is Nonlinear



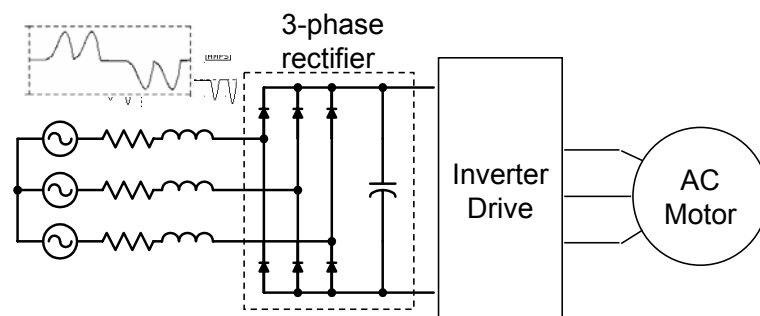
Used for:
Computers,
Printers, Fax,
most ITE
Electronic Lighting
Communications
Food Preparation



Used for:
HVAC, Battery
Charging, Food
Preparation,
Elevators

62

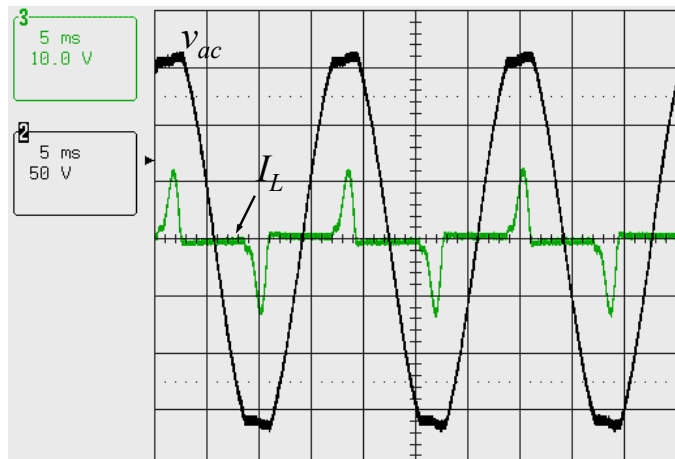
Inverter Output Voltage Under Nonlinear Rectifier Load



- Single-phase nonlinear load current is rich with odd harmonics (3,5,7,...) especially with the 3rd harmonic
- The voltage waveform is flattened up due to nonlinear current.

63

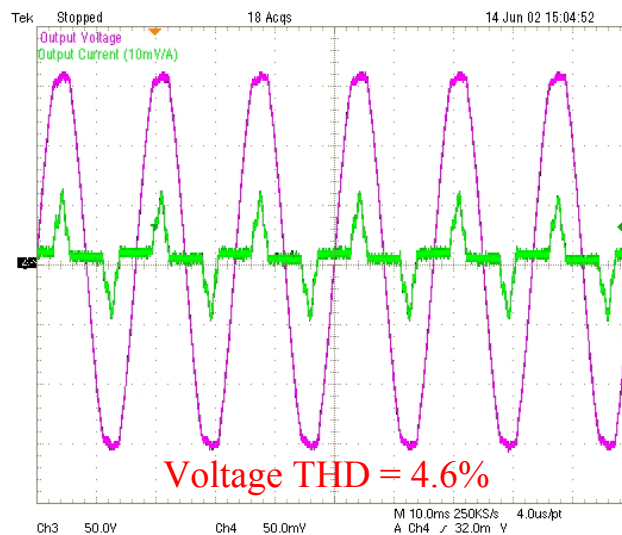Voltage Waveform Quality may be Improved with Closed-loop Control



Closed-loop control can smooth the voltage waveform but the nonlinear current waveform remains nasty.


64

6. Fuel Cell and Converter Interactions

- Static modeling
- Dynamic modeling
- Fuel cell dynamic response with and without converters

65

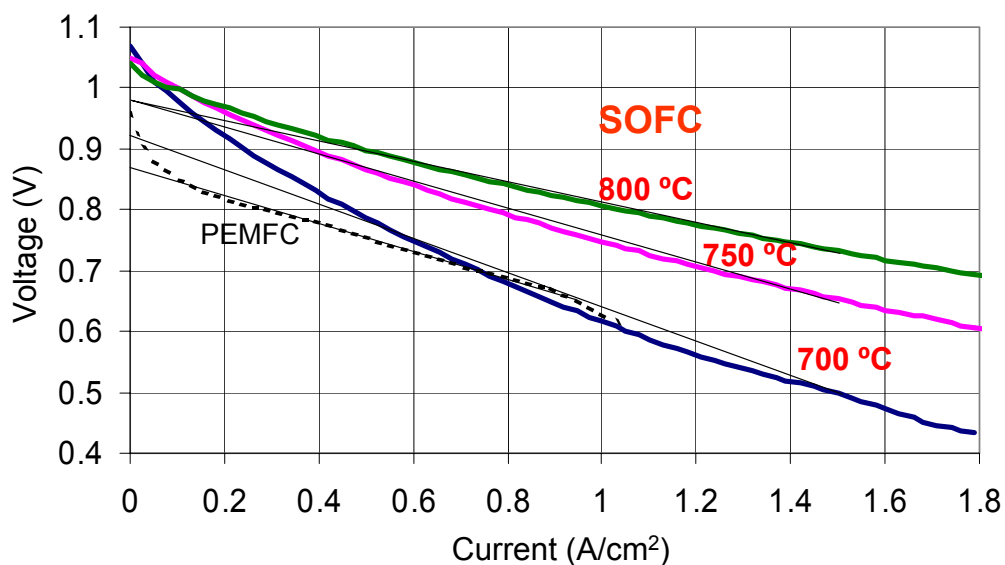
SOFC Voltage-Current Characteristic as a Function of Temperature



Data source: DOE SECA Modeling team report at Pittsburgh Airport, 10/15/2002


66

Power Density of SOFC and PEMFC

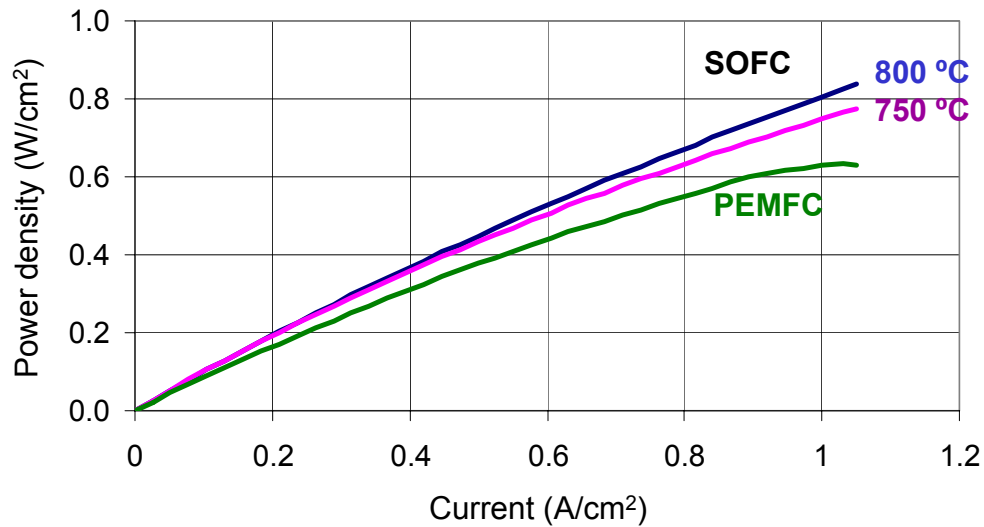


67

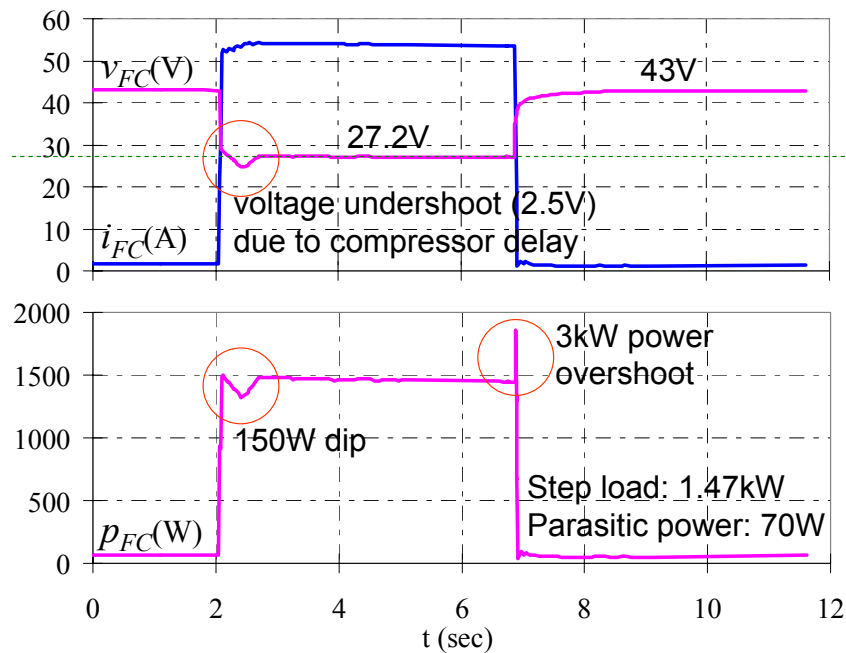PEM Fuel Cell Dynamic Characteristics Nexa 1.2kW Unit




68

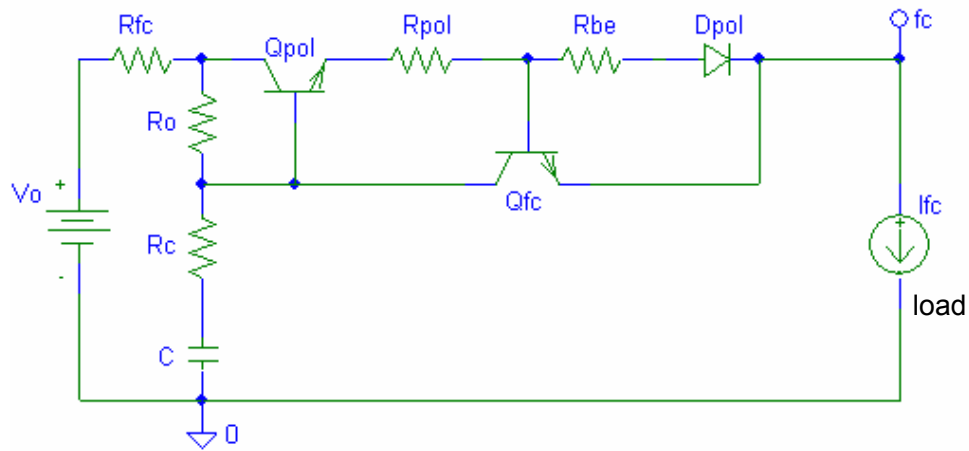Fuel Cell Modeling with Electrical Circuit




69

Nexa1200 Polarization Curve

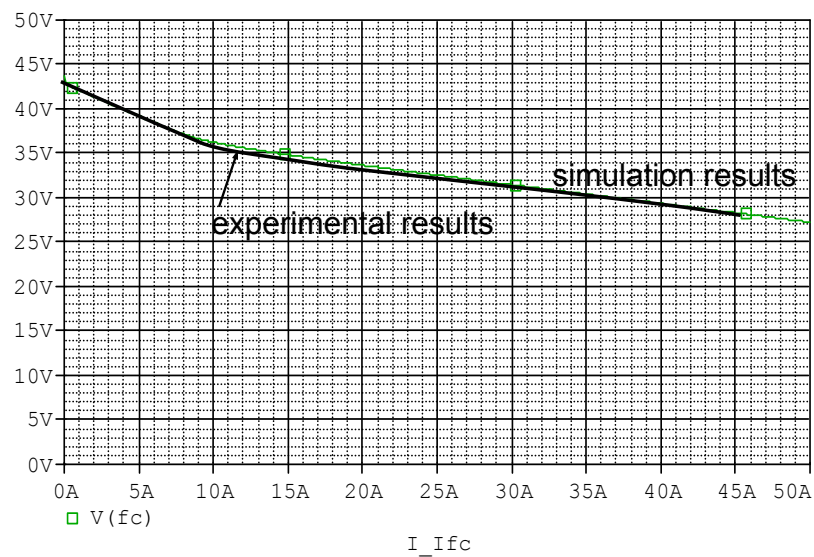


70

Polarization Curves for Nexa PEM FC

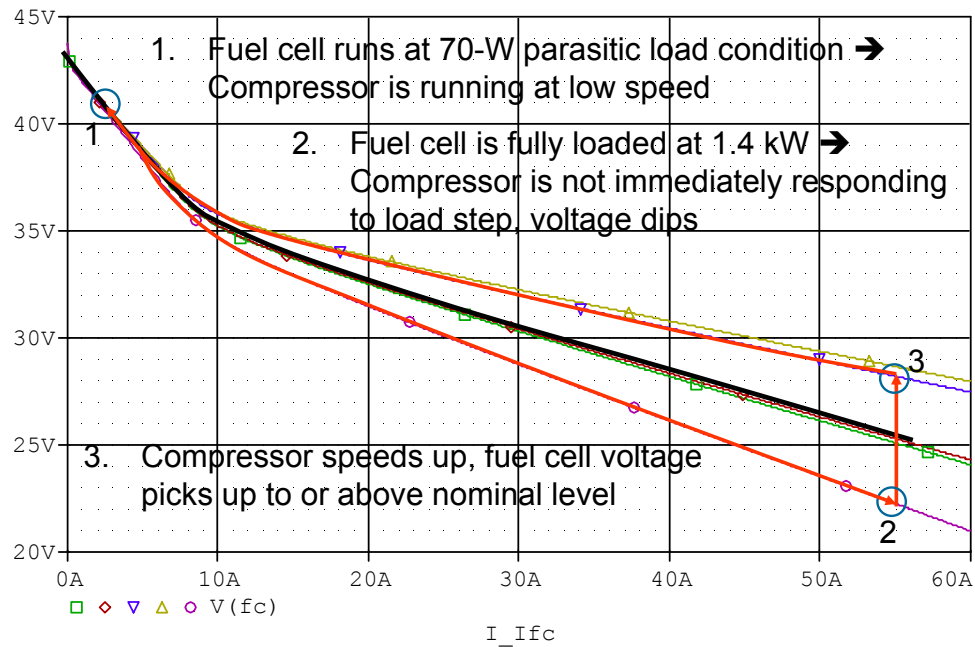

71


Time Domain Response

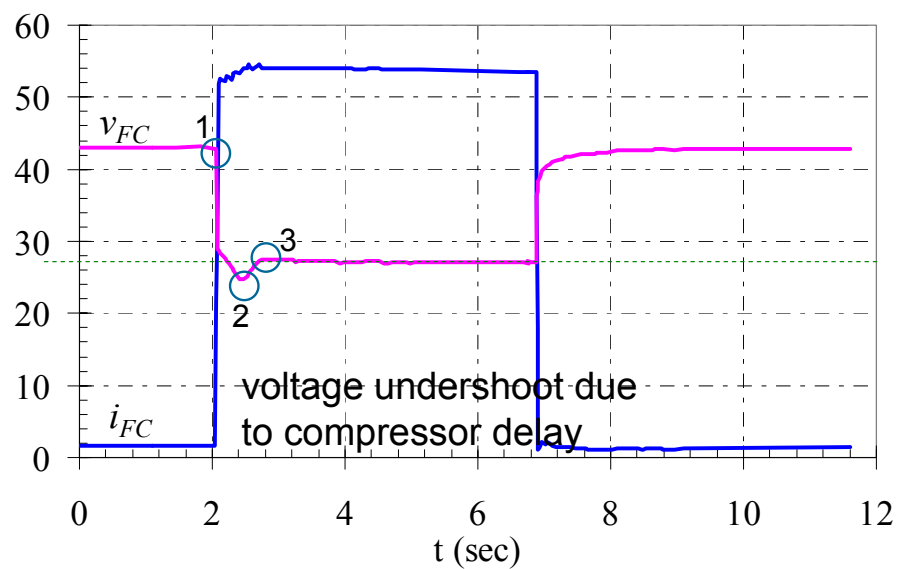

72

PEM Fuel Cell Dynamic Simulation Diagram

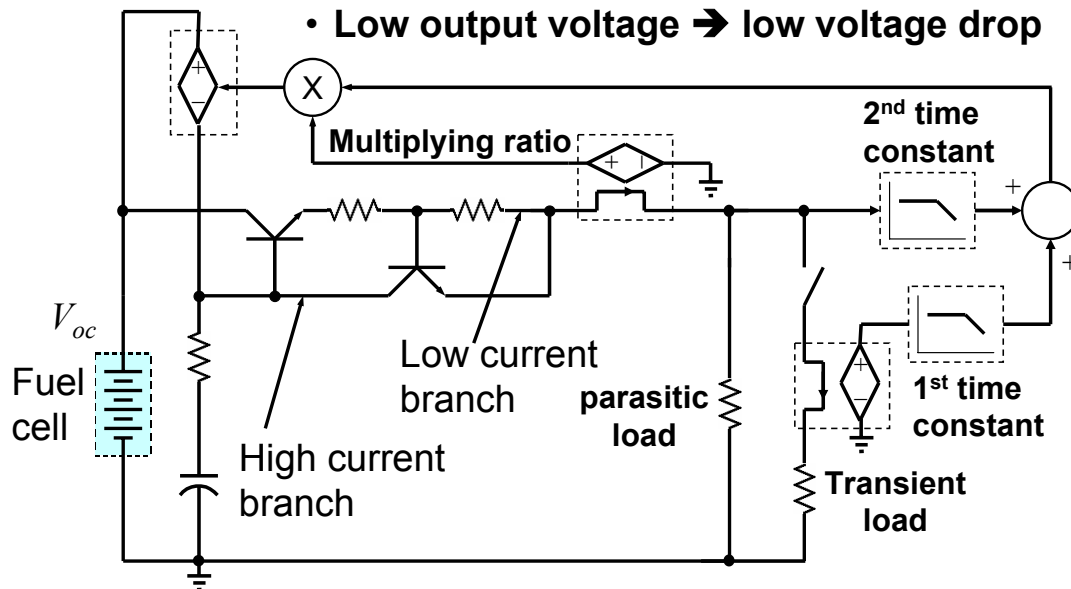
- High load current → high voltage drop
- Low output voltage → low voltage drop




73

Fuel Cell Stack Output Dynamic Simulation and Experimental Results

(a) experimental results

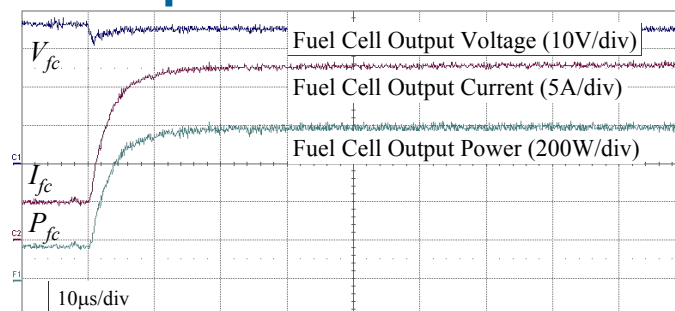


(b) simulation results

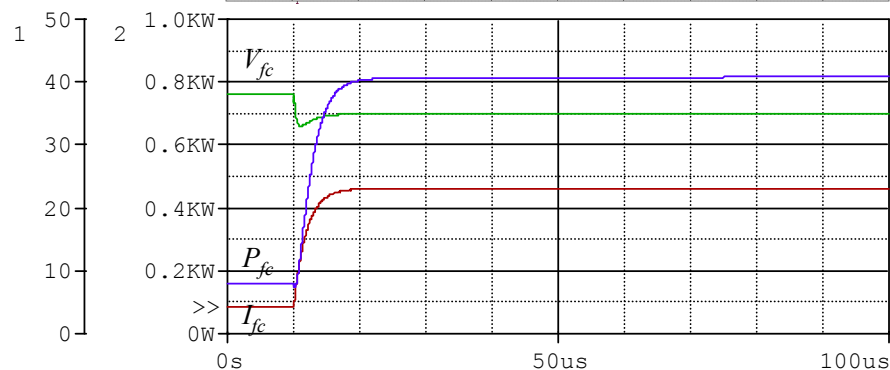


74

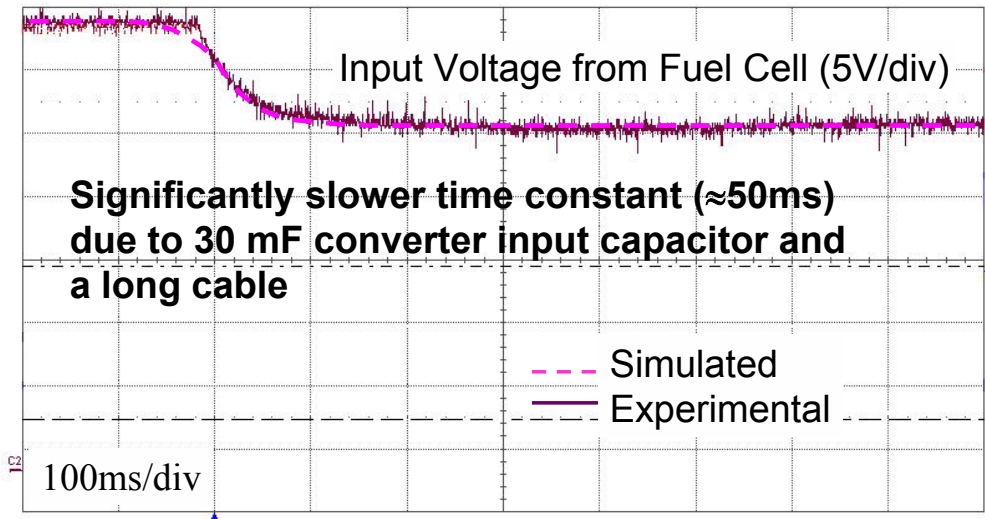Fuel Cell Voltage Dynamic with Converter Load Transient




75

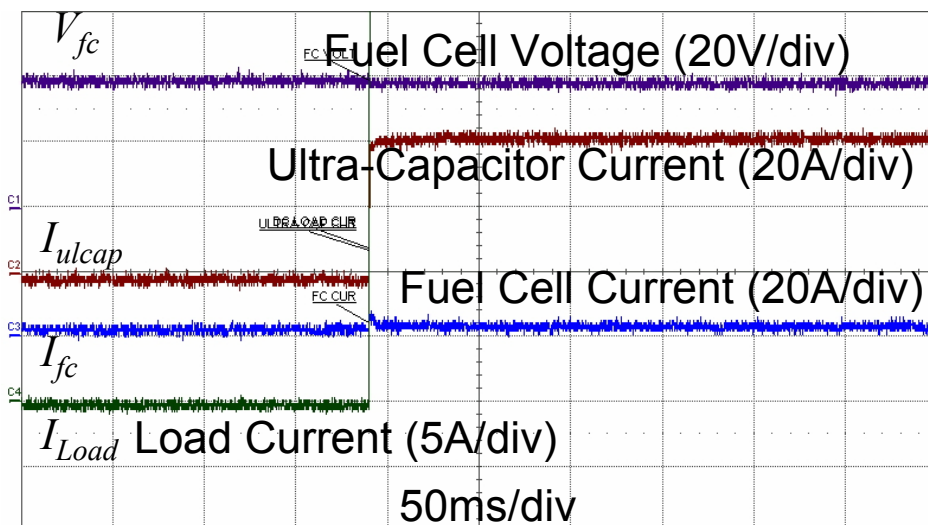Fuel Cell Responds with a Paralleled 140F Ultra Capacitor Capacitor



76

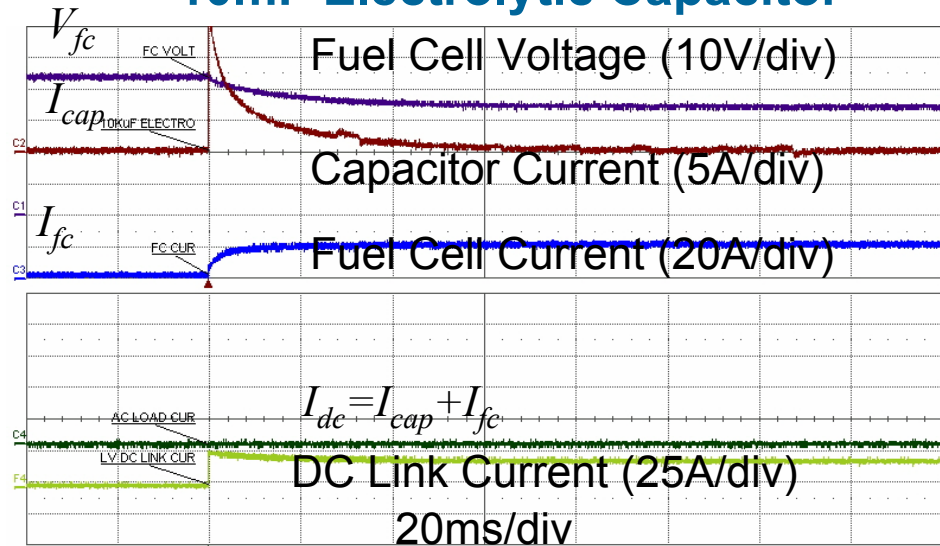Fuel Cell Responds with a Paralleled 10mF Electrolytic Capacitor



Note: Fuel cell output voltage response is slowed down to 30ms. Capacitor takes over the transient current.

77

Findings of Fuel Cell Modeling and Converter Test Results

- Fuel cell stack shows very fast dynamic, nearly instantly without time constant
- Perception of slow fuel cell time constant is related to ancillary system not fuel cell stack
- Output voltage dynamic is dominated by the converter interface capacitor and cable inductor
- Output current dynamic is dominated by the load

78

Issues to be Resolved in a Fuel Cell Power Conditioning System

- **Energy management** system options – Sizing of converters and auxiliary sources
- Advanced **Bidirectional dc-dc converter** technologies
- **Interleaved control** and associated technologies
- **Digital control** for high power dc/dc converters
- Fuel cell **voltage standardization**
- Fuel cell **ripple current specifications**
- Fuel cell **output voltage dynamic**
- Fuel cell and power conditioning **interface and communication protocol**

7. Fuel Cell Energy Management Issues

- Problems without Slow Fuel Cell Response and Auxiliary Energy Storage
- Options of Energy Storage Placement
- Energy Management options with Bidirectional DC/DC Converters


Why Fuel Cells Need **Auxiliary** Energy Source or Energy Storage?

- For **standalone** power supplies: need energy storage for load transient
- For **grid-connected** power supplies: need auxiliary energy source for start-up
- For all systems: need auxiliary energy source to provide power for control signals

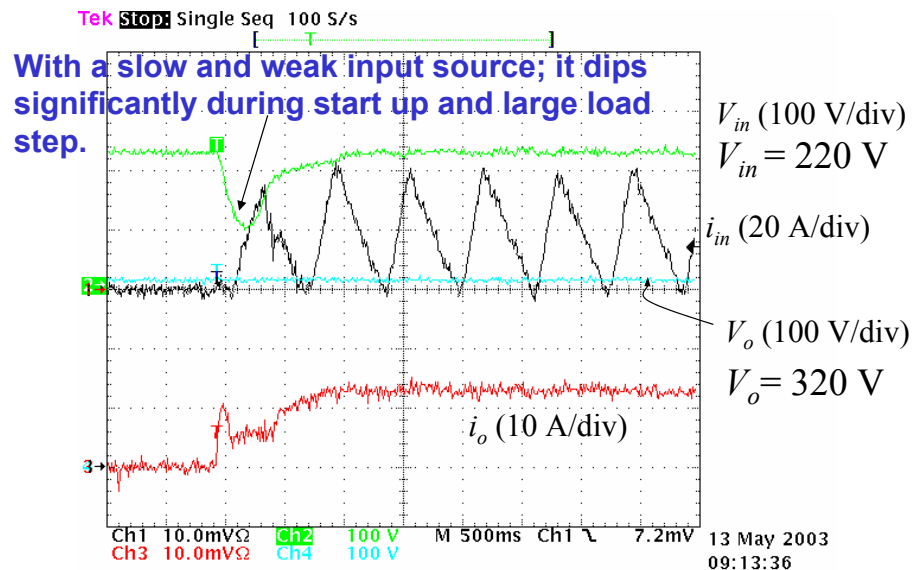Problems of a Fuel Cell System without Energy Storage


- Fuel cell does not have storage capability
- **Slow response**, output voltage fluctuates with loads
- Source may not be continuously available
- Size (or capacity) needs to be higher than the peak load
- When sized enough for the maximum load, excess **energy will be wasted**

A Slow and Weak Energy Source During Startup and Large Load Transient



83

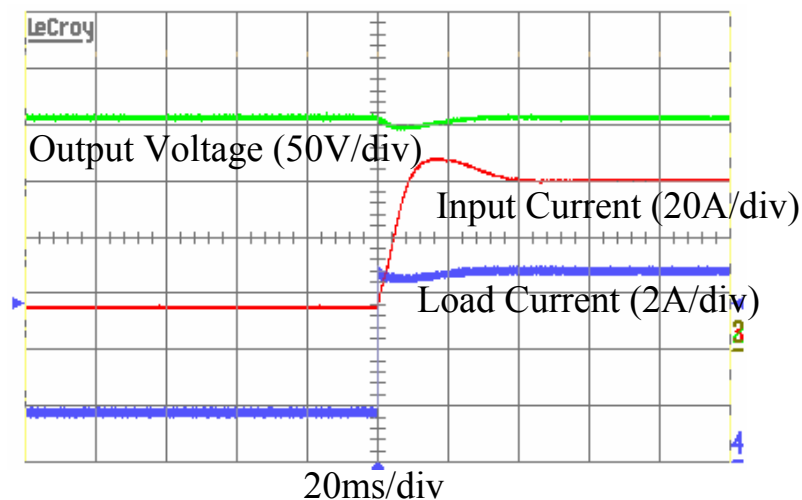
Converter Step Load Response with Stiff Voltage Source and Voltage Loop Control



With voltage control loop bandwidth designed at 20 Hz, settling time is about 40ms under load step

84

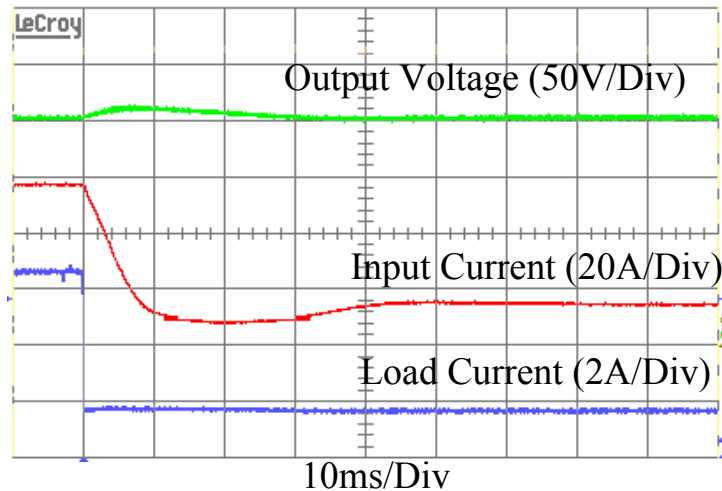
Converter Load Dump Response with Stiff Voltage Source and Voltage Loop Control



With voltage control loop bandwidth design at 20 Hz, settling time is about 40ms under load dump

85

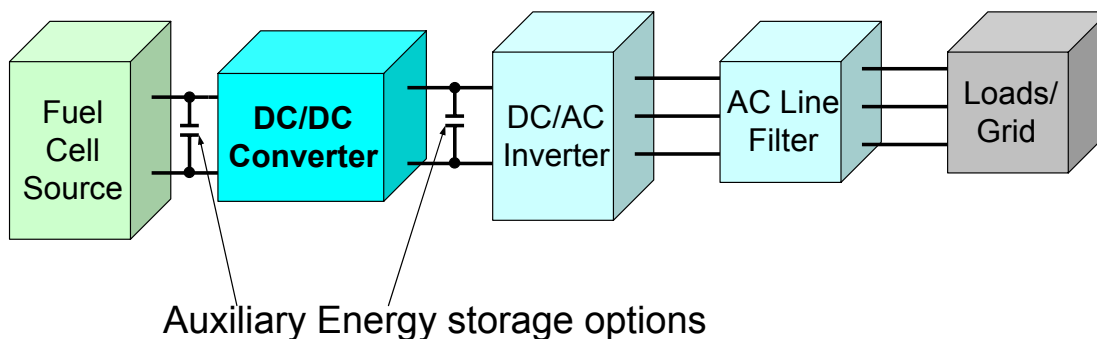
A Fuel Cell Power Plant with Energy Storage



Fuel Cells Need **Auxiliary Energy Storage** for energy management


86

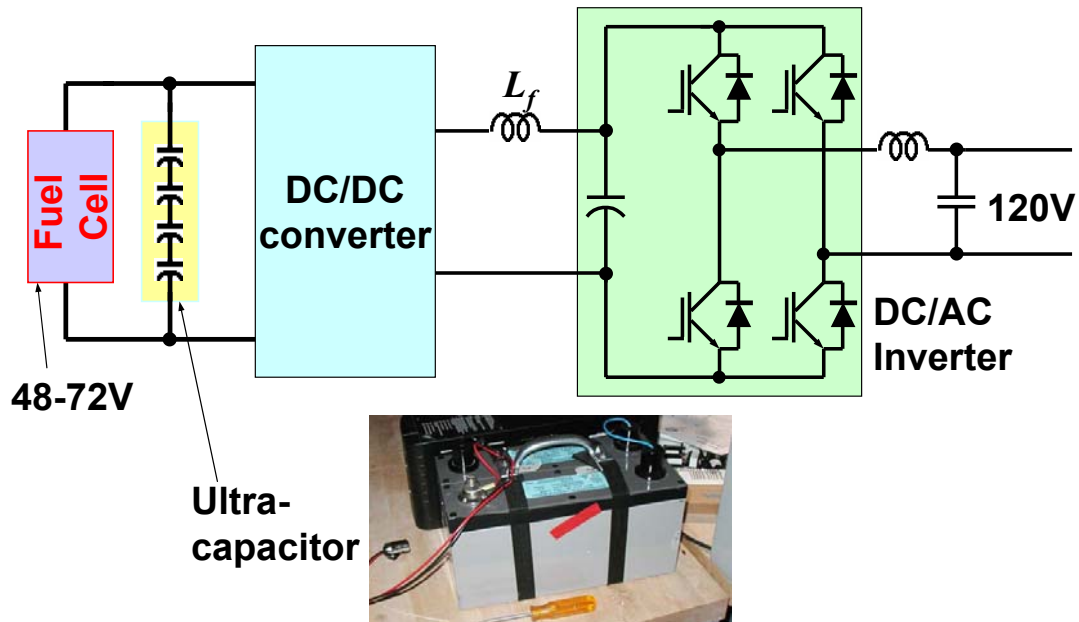Low-Voltage Ultra-Capacitor Energy Storage Configuration



87

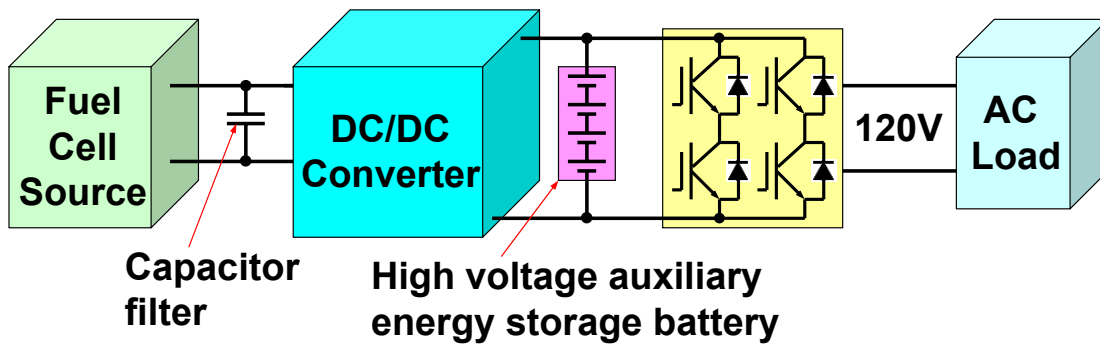Use High-Voltage Battery as the Auxiliary Energy Storage



fuse

Photograph
of a 96V
battery bank

88

Potential Problems with Passive Energy Storage

- **Low-side ultracap option:**
 - Two voltage sources are paralleled – not a good engineering practice
 - Time to reach equilibrium point is too long because dynamic characteristics of both sources are different
 - Ultra capacitor helps transient current sharing, but creates significant voltage and current ripples due to interaction between two voltage sources
 - Dynamic current sharing problem
- **High-side battery option:**
 - Battery cell voltage balance problem
 - Battery state-of-charge management
 - Long-term battery life expectancy
 - Cost of battery is a concern

Energy Management Options with Energy Storages and Power Electronics


- Optimum energy usage control
- Start-up control
- Load transient control
- Charging and discharging (bidirectional) controls for auxiliary energy storages

Design Considerations for Hybrid-Source Systems

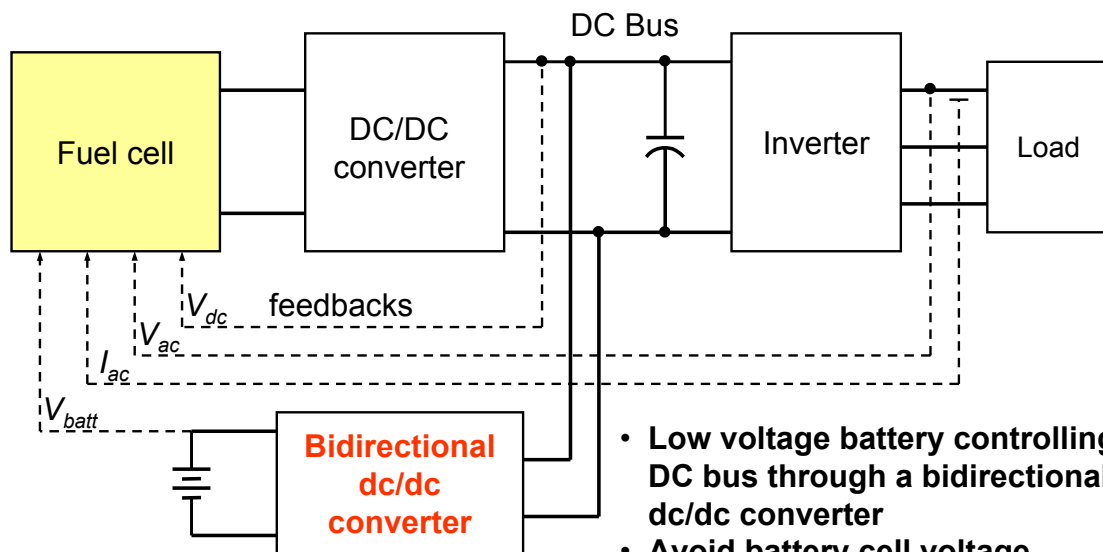1. **Utilization** of Primary Source
2. **Simple Power Circuit** (as simple as possible)
3. Voltage ratio
4. **Isolation** Requirement
5. **Energy Storage** Requirement
6. Inverter **DC Bus Voltage** Requirement
7. **Cost**

91


Energy Management Using Low Voltage Battery and Bidirectional DC/DC



- Low voltage battery controlling DC bus through a bidirectional dc/dc converter
- Avoid battery cell voltage balancing problem
- Complicated control

92

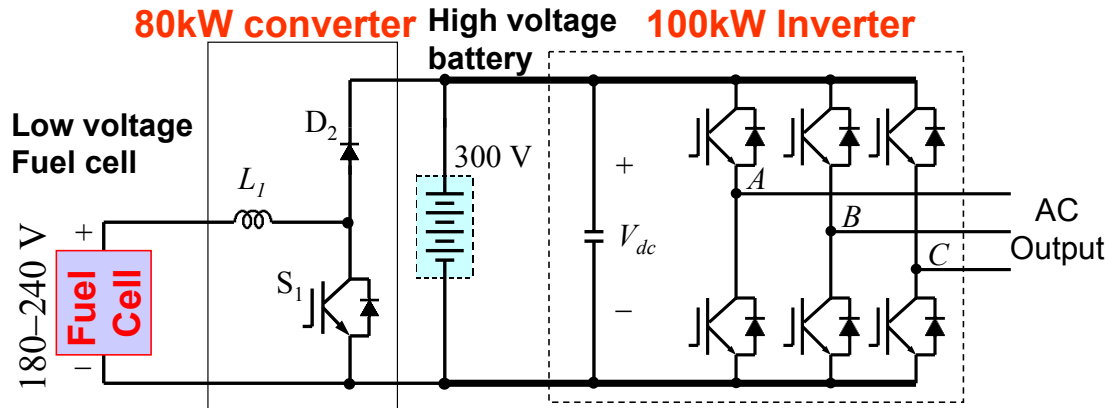Dual-Source Energy Management Using a Unidirectional Boost Converter




- Battery voltage > Fuel cell voltage
- Simple boost converter regulates the battery state of charge
- DC bus voltage is constant

Total power electronics: 80-kW DC/DC + 100-kW DC/AC
 Total energy sources: 20-kW battery + 80-kW fuel cell

93

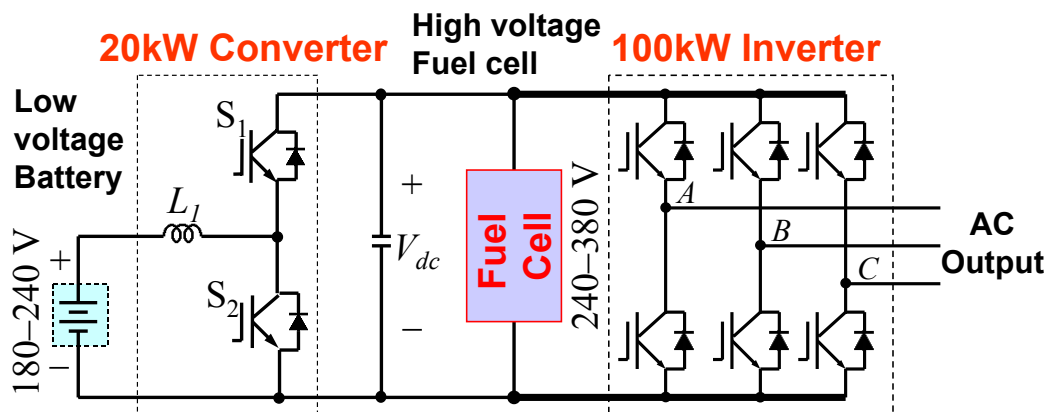An Example of Dual Sources with a Bidirectional DC-DC Converter




Battery voltage < fuel cell voltage → needs a boost converter to supply energy during transient load and a buck converter to charge the battery
 Fuel cell voltage = dc bus voltage → not regulated

- Total power electronics: 20-kW DC/DC + 100-kW DC/AC
- Total energy sources: 20-kW battery + 80-kW fuel cell

94

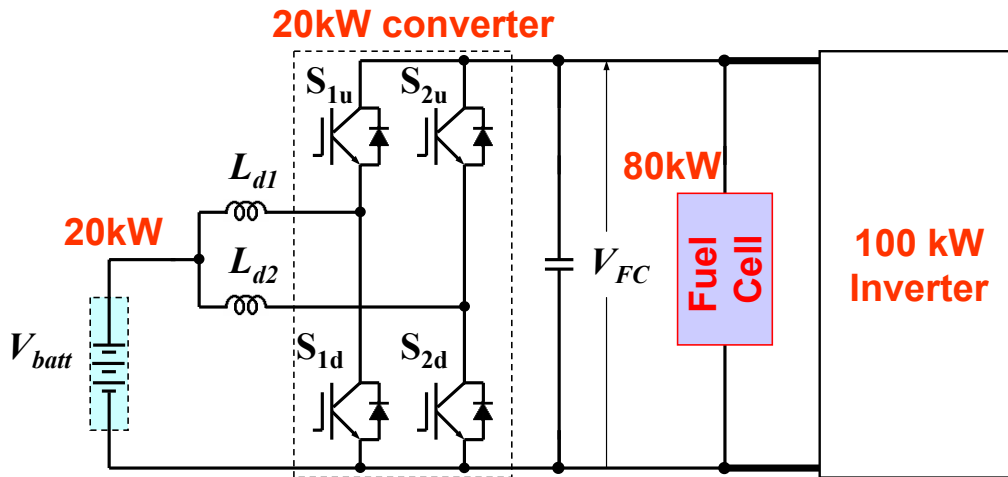Interleaved Bidirectional DC/DC Converter for Fuel Cell Energy Management




Interleaved operation for both boost and buck modes →

- smaller passive components;
- less battery ripple current
- Total power electronics: 20-kW DC/DC + 100-kW DC/AC
- Total energy sources: 20-kW battery + 80-kW fuel cell

95

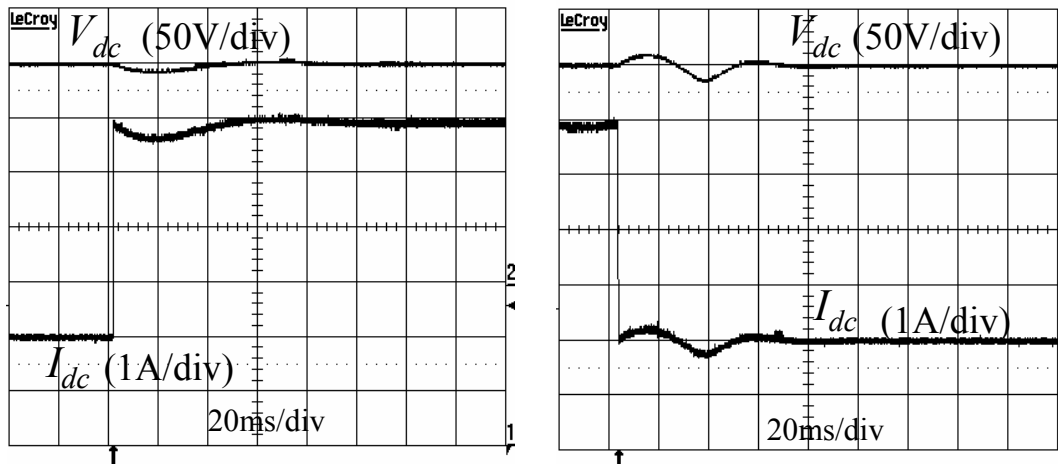
DC Bus Voltage During 800-W Load Step and Load Dump Under Boost Mode Operation



DC bus voltage fluctuates but returns to original setting after load transients

96

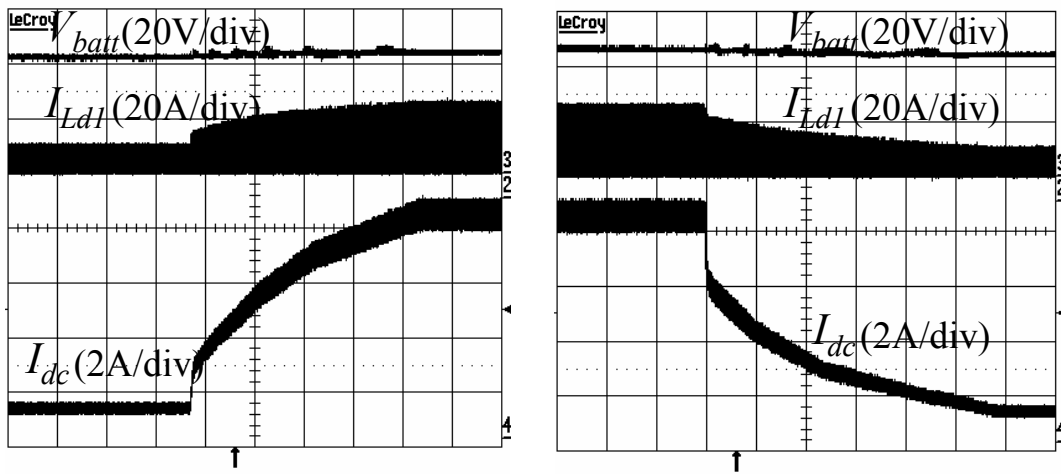Battery Voltage During 800-W Battery Charge Command Step under Buck Mode Operation



Battery voltage keeps constant during severe charging and discharging current conditions


97

8. Advanced V6 Converter

- Single-Phase Half-Bridge Converter
- Two-Phase Full-bridge Converter
- Three-Phase Converter
- V6 Converter
- Test Results with V6 Converter
- V6 Converter Prototype


98

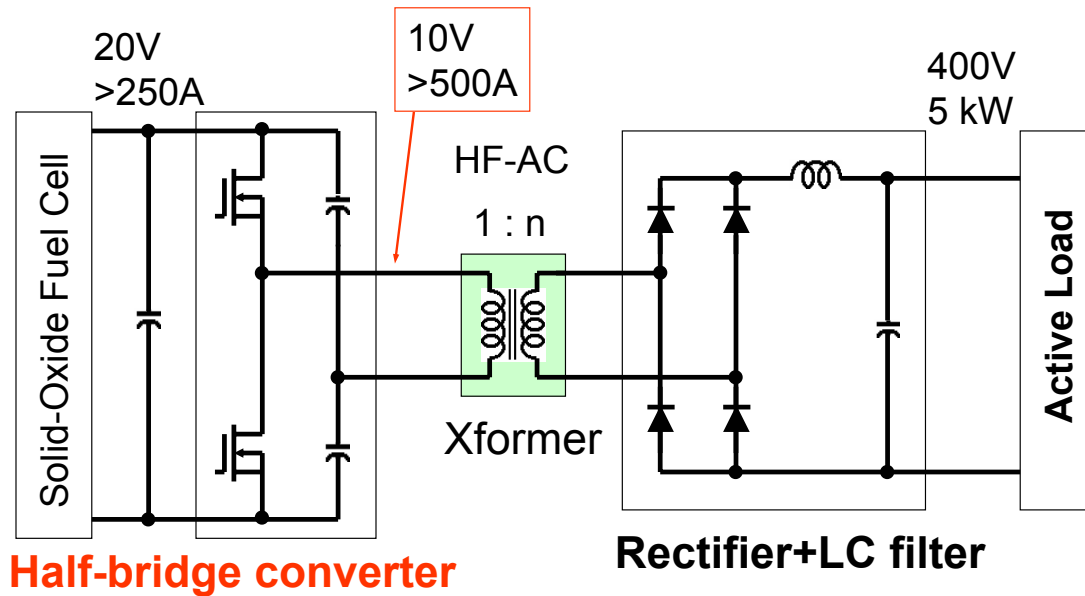Half-Bridge Converter – A Single-Phase Converter




99

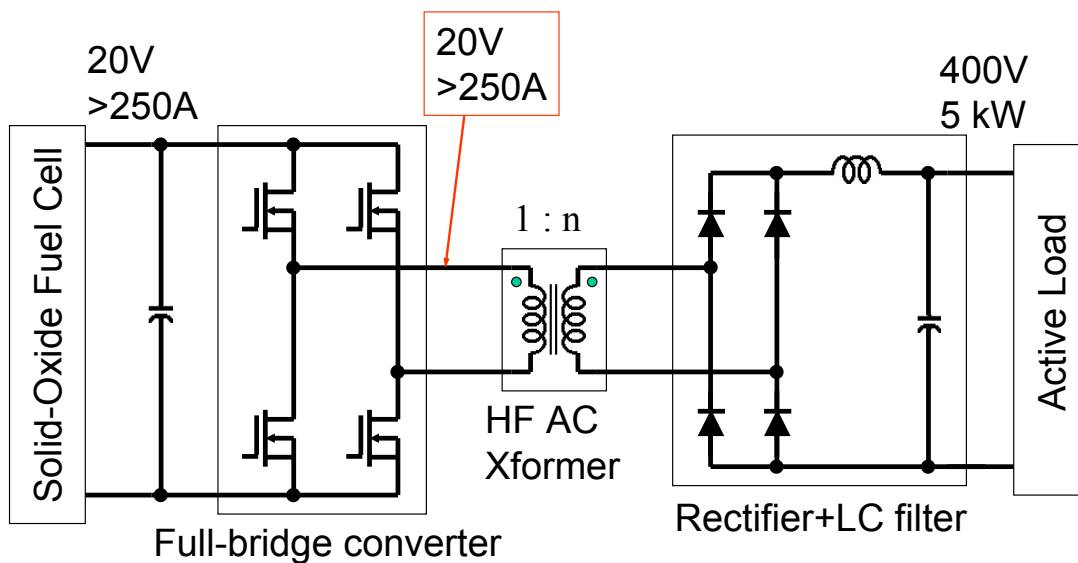Full-Bridge Converter – A Two-Phase Converter



100

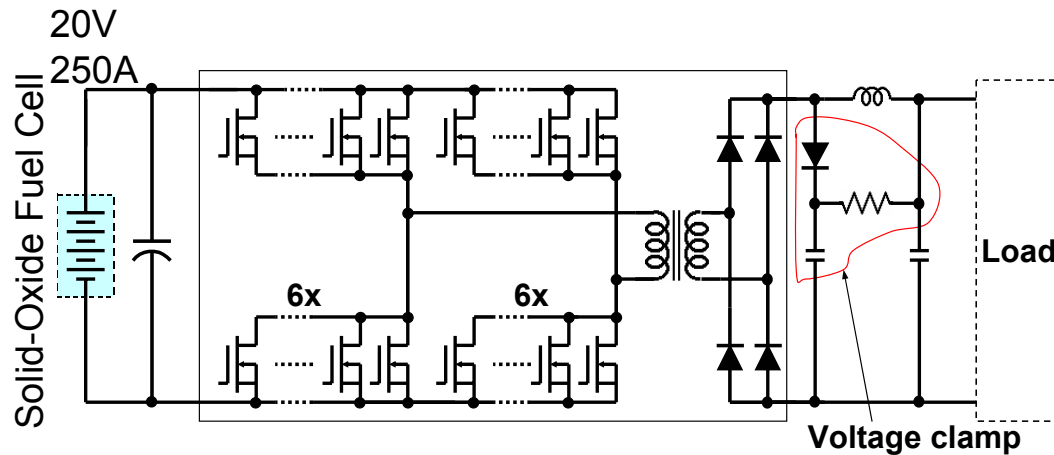
Full-Bridge Converter with Paralleled Devices to Achieve Desired Power Levels



- With 6 devices in parallel, the two-leg converter can barely achieve 95% efficiency
- Problems are additional losses in **parasitic components, voltage clamp, interconnects, filter inductor, transformer, diodes, etc.**


101

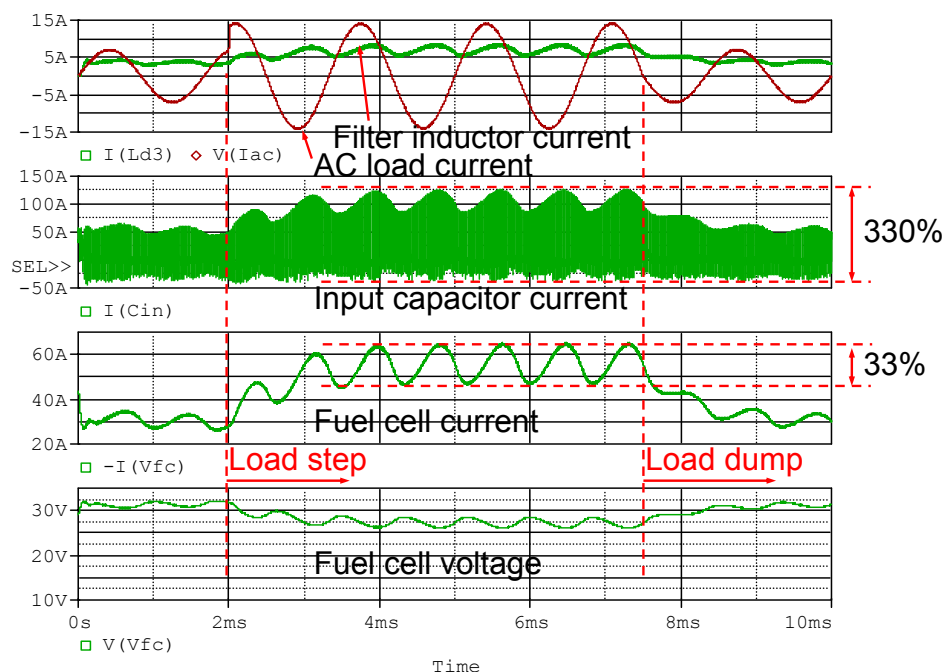Fuel Cell Voltage and Current with Full Bridge Converter Case




102

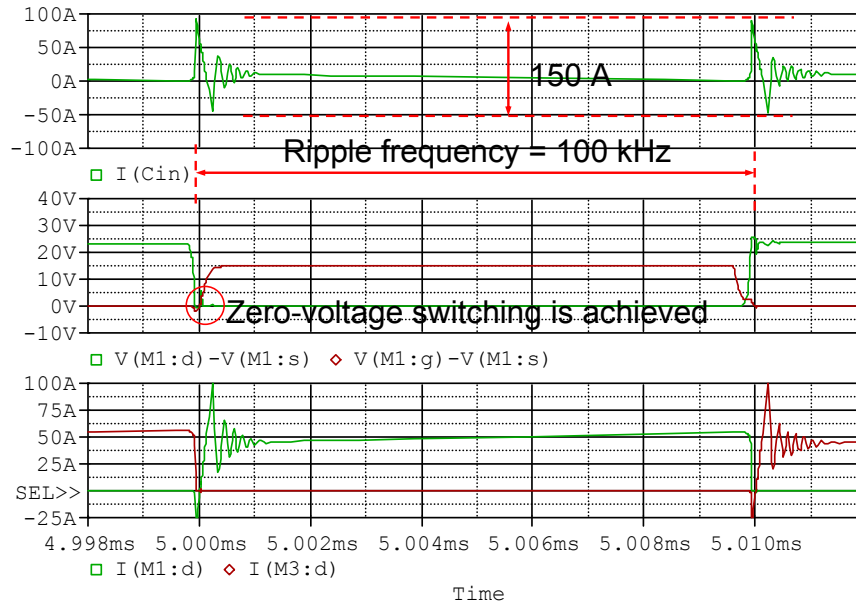Switching Waveforms with Full-Bridge Converter



103


A Three-Phase Bridge Converter

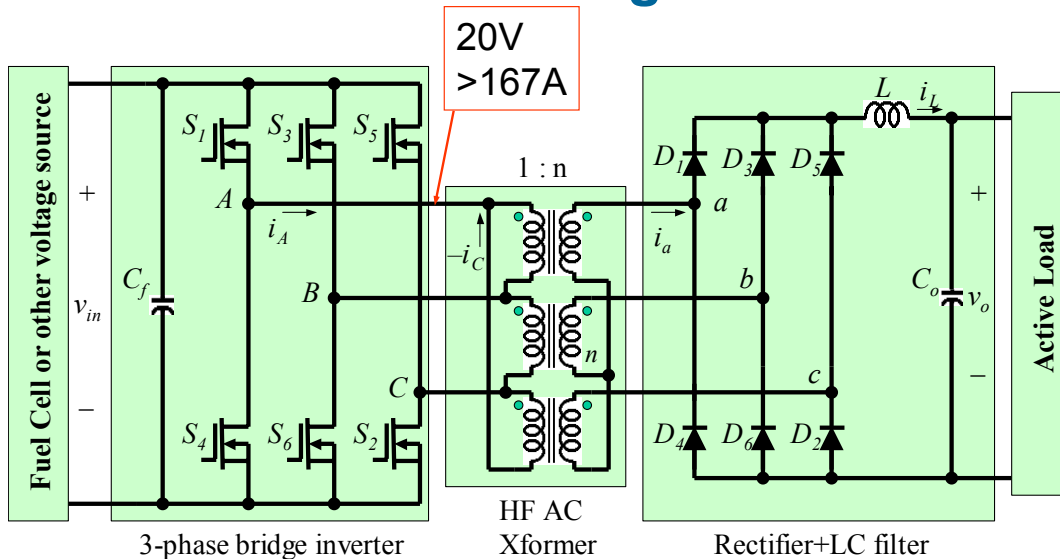

- Hard switching
- With 4 devices in parallel per switch
- Efficiency $\approx 95\%$


104

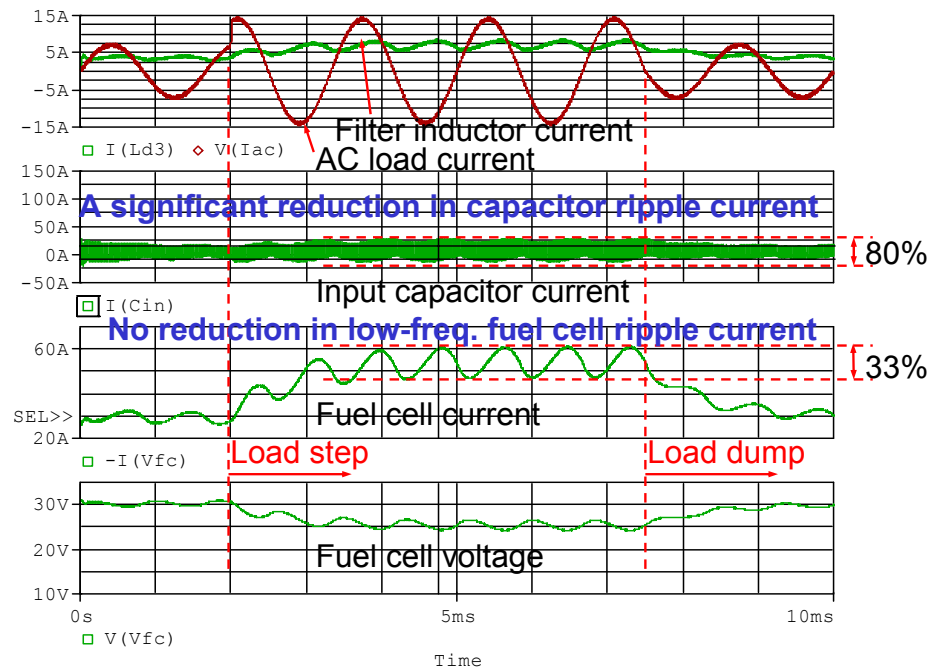Fuel Cell Voltage and Current with 3-Phase Bridge Converter Case



105

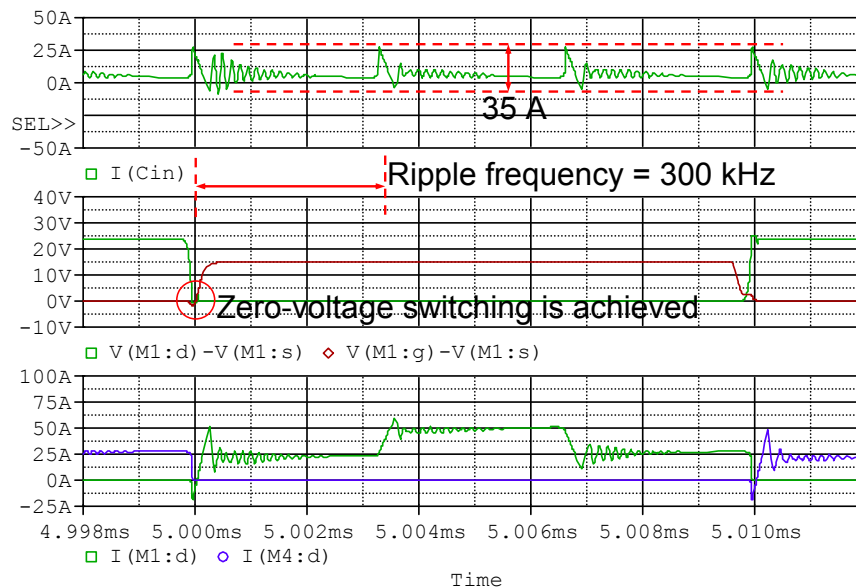Switching Waveforms with 3-Phase Bridge Converter




106

Key Features of Multiphase Converter

- Device is switched at a lower current, while maintaining zero-voltage switching.
- High-frequency capacitor ripple current is reduced by $>4x$, and its frequency is increased by $3x$. This translates to significant capacitor size reduction and cost saving.
- No effect on low-frequency AC current ripple, which remains an issue to be solved.

107

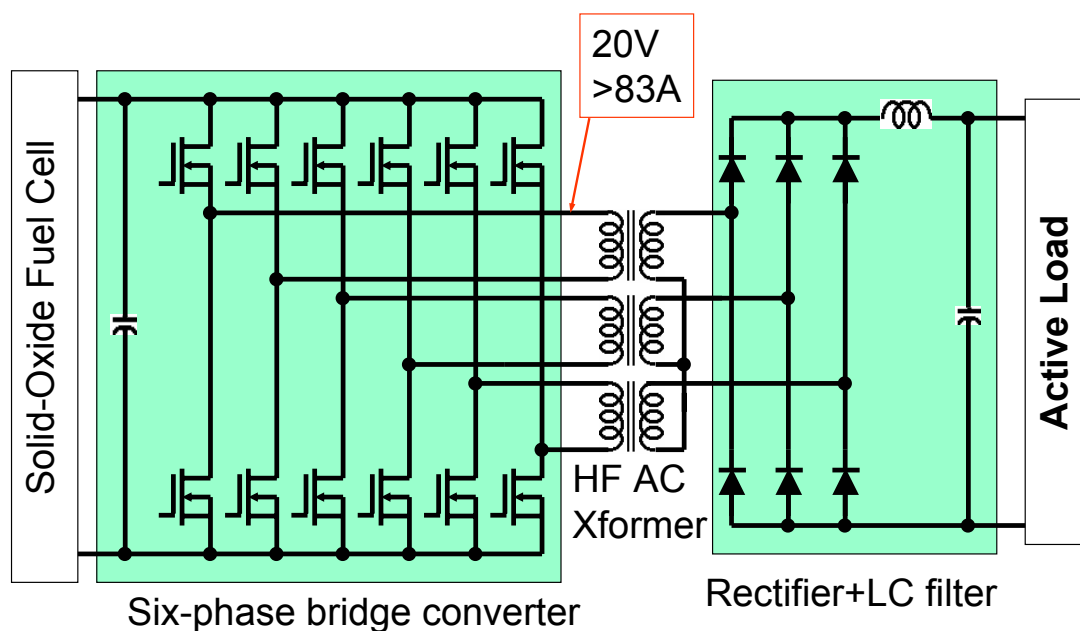Circuit Diagram of the Virginia Tech V6 Converter





108

Key Features of V6 Converter

- Double output voltage → reduce turns ratio and associated leakage inductance
- No overshoot and ringing on primary side device voltage
- Input side high-frequency ripple current elimination → cost and size reduction on high-frequency capacitor
- Output DC link inductor current ripple elimination → cost and size reduction on inductor
- Secondary voltage overshoot reduction → cost and size reduction with elimination of voltage clamping
- Significant EMI reduction → cost reduction on EMI filter
- Soft switching over a wide load range
- High efficiency ~97%
- Low device temperature → High reliability

109

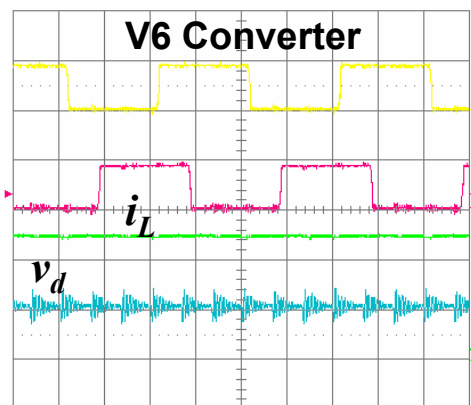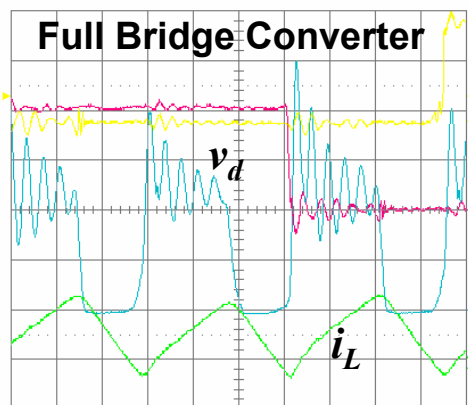
Waveform Comparison between Full-Bridge and V6 Converters



- Secondary inductor current is ripple-less; and in principle, no dc link inductor is needed
- Secondary voltage swing is eliminated with <40% voltage overshoot as compared to 250%

110

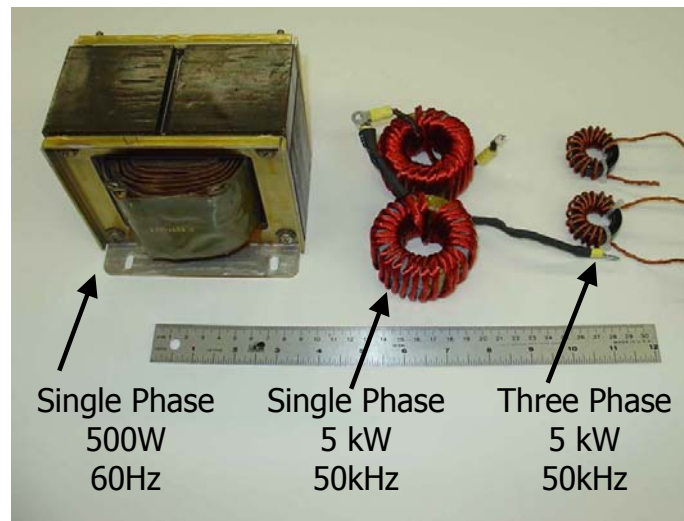
Significant DC link Inductor Size Reduction




With V6 converter, an effective 10x reduction in DC link filter inductor in terms of cost, size and weight

111

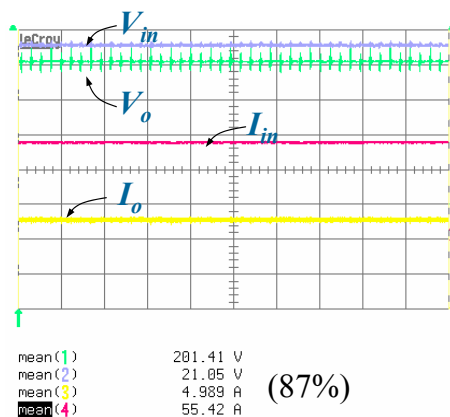Input and Output Voltages and Currents at 1kW Output Condition



(a) Full bridge converter

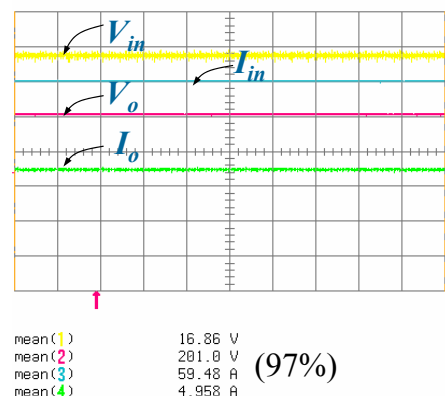

(b) V6 Converter


Significant improvement with V6 converter

- ✓ Less EMI
- ✓ Better efficiency (97% versus 87% after calibration)

112

Where are the Losses?

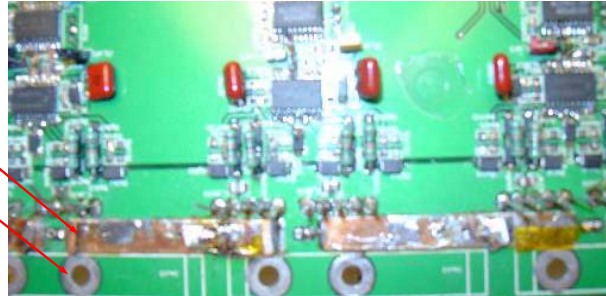
- Switch conduction
- Diode conduction
- Transformer
- Output rectifier
- Output filter inductor and capacitor
- Input capacitor
- Parasitics
 - Copper traces
 - Interconnects




Calorimetry for Accurate Loss Measurement



Calibration with resistor bank

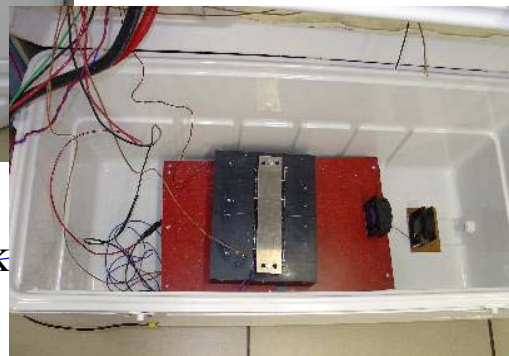


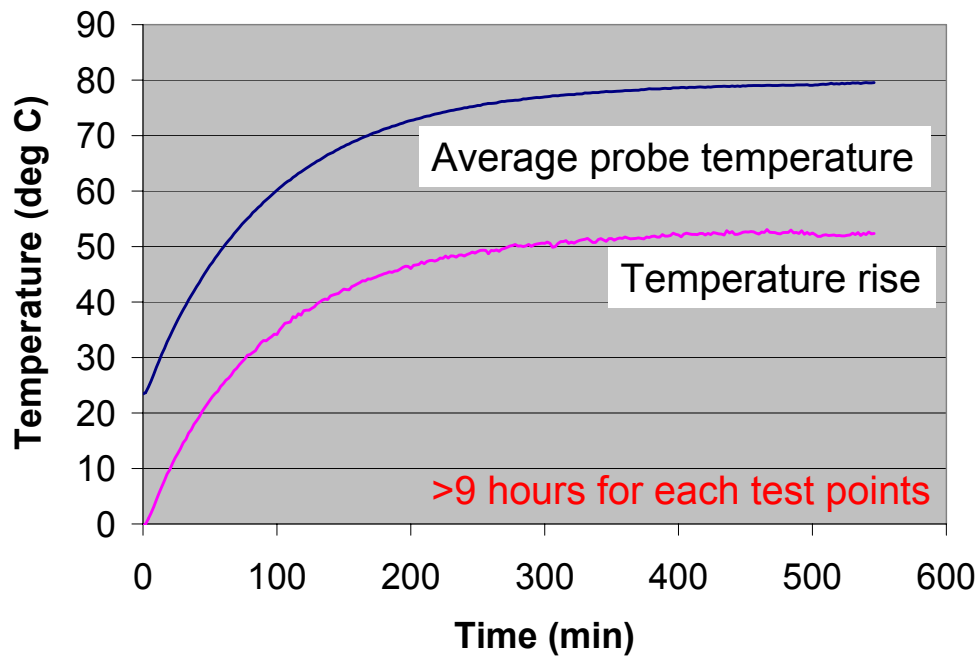Test the 160-Liter Calorimeter at 120-W Loss Condition




115

Temperature Rise Versus Power Loss

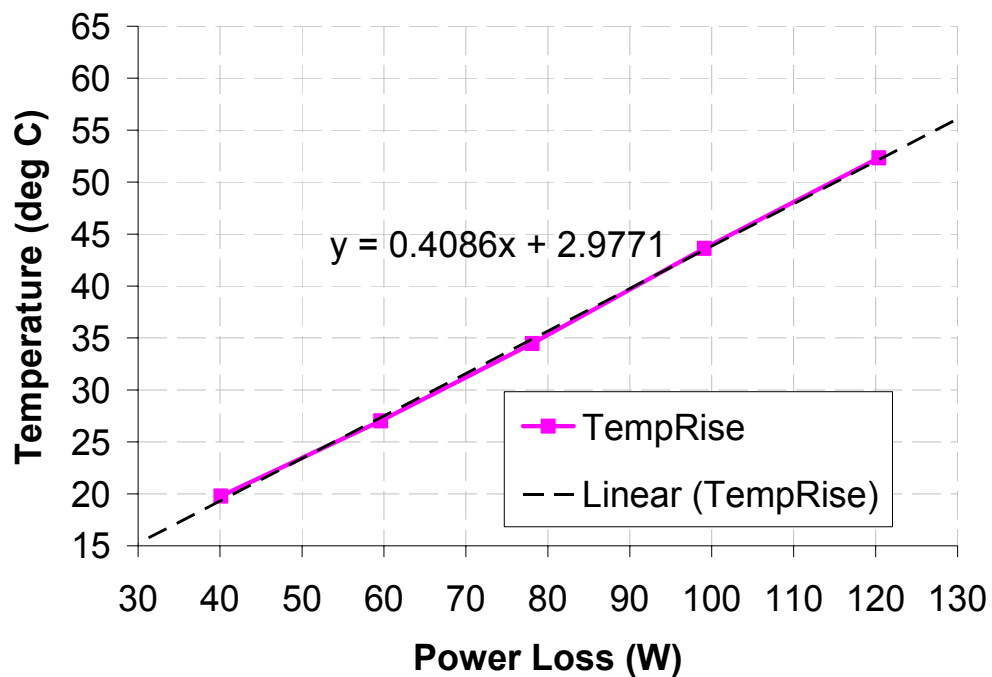

116

Efficiency Measurement Results

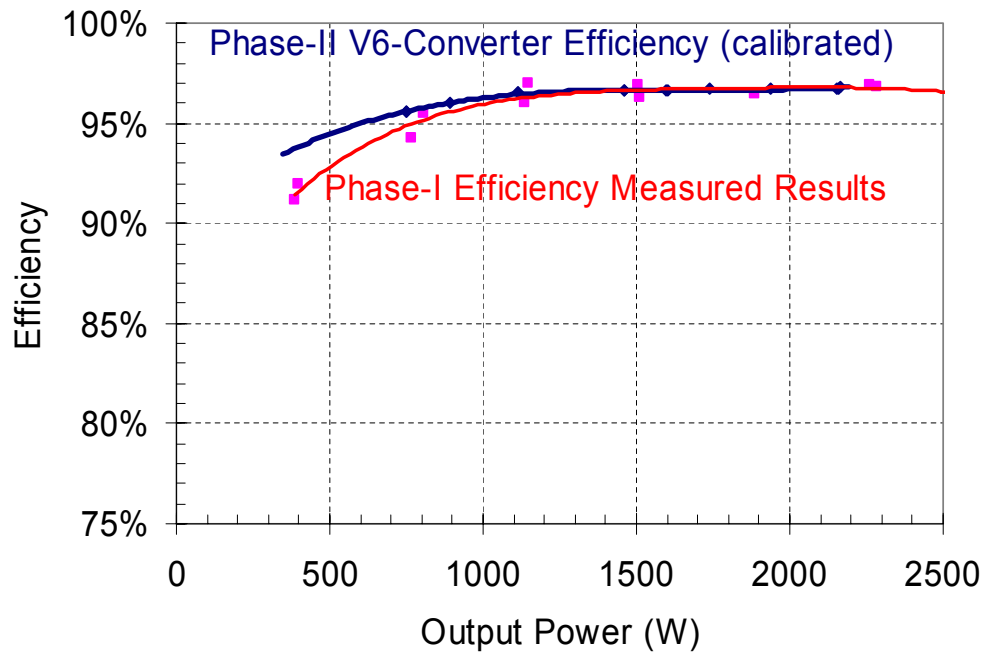


117

The Beta Version Prototype Converter

- Schematic Circuit Diagrams
- V6 Cost Estimate
- Summary of Beta Version Prototype


118

Schematic Circuit Diagrams

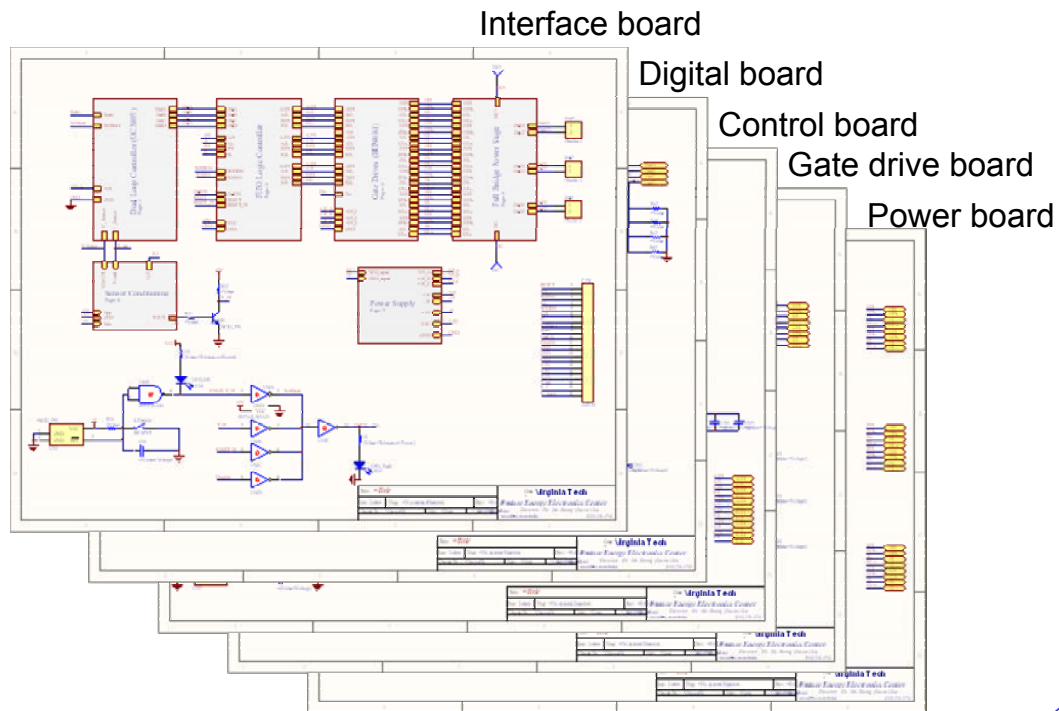

119

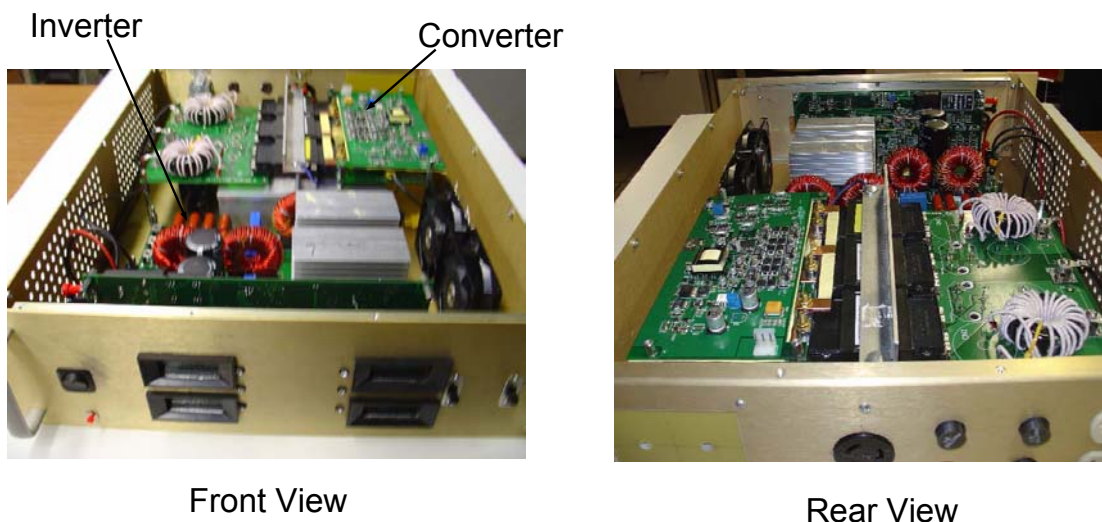Photographs of V6-Converter Together with DC-AC Inverter Prototype



120


Prototype and Production Cost Estimate for the 5-kW V6 DC-DC Converter

| Quantity | 100 | 1000 | 10000 |
|-----------------------------|---------|-------|-------|
| Material cost | \$475 | \$347 | \$227 |
| Tooling, Assembly & Testing | \$1,424 | \$347 | \$114 |
| Production Cost | \$1,899 | \$694 | \$341 |

| Key Materials | Parts Count | Qty 1 | Qty 10000 |
|-----------------|-------------|----------|-----------|
| Power Circuit | 22 | \$571.00 | \$154.40 |
| Devices | 8 | \$201.00 | \$38.40 |
| Capacitors | 6 | \$84.00 | \$30.00 |
| Transformers | 3 | \$180.00 | \$45.00 |
| Inductors | 2 | \$24.00 | \$8.00 |
| Sensors | 2 | \$32.00 | \$8.00 |
| Contactors | 1 | \$50.00 | \$25.00 |
| Control Circuit | 325 | \$113.70 | \$33.22 |
| Resistors | 164 | \$18.59 | \$2.71 |
| Capacitors | 110 | \$46.61 | \$17.41 |
| Discretes | 27 | \$8.00 | \$2.42 |
| IC's | 24 | \$40.50 | \$10.68 |
| Miscellaneous | 55 | \$174.80 | \$52.44 |
| Total | 402 | \$840.50 | \$227.05 |

121

9. Fuel Cell Current Ripple Issues

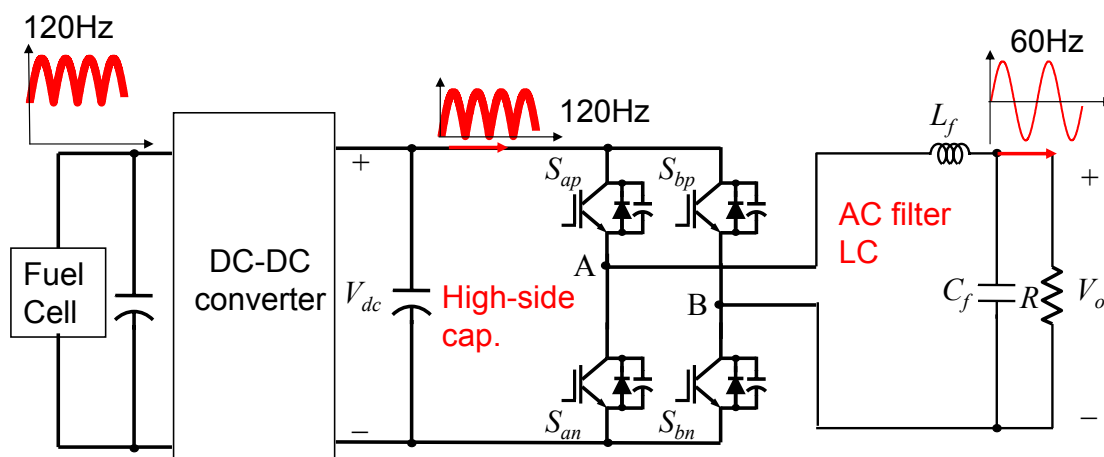

- Current ripple propagates from AC load back to DC side
- With rectification, ripple frequency is 120 Hz for 60 Hz systems
- Low-frequency ripple is difficult to be filtered unless capacitor is large enough


122

AC Current Ripple Problems

- Inverter AC current ripple propagates back to fuel cell
- Fuel cell requires a higher current handling capability
→ **Cost penalty to fuel cell stack**
- Ripple current can cause hysteresis losses and subsequently more fuel consumption → **Cost penalty to fuel consumption**
- State-of-the-art solutions are adding more capacitors or adding an external active filters → **Size and cost penalty**
- Virginia Tech solution is to use existing V6 converter with active ripple cancellation technique to eliminate the ripple → **No penalty**

123

Circuit Model for AC Current Ripple

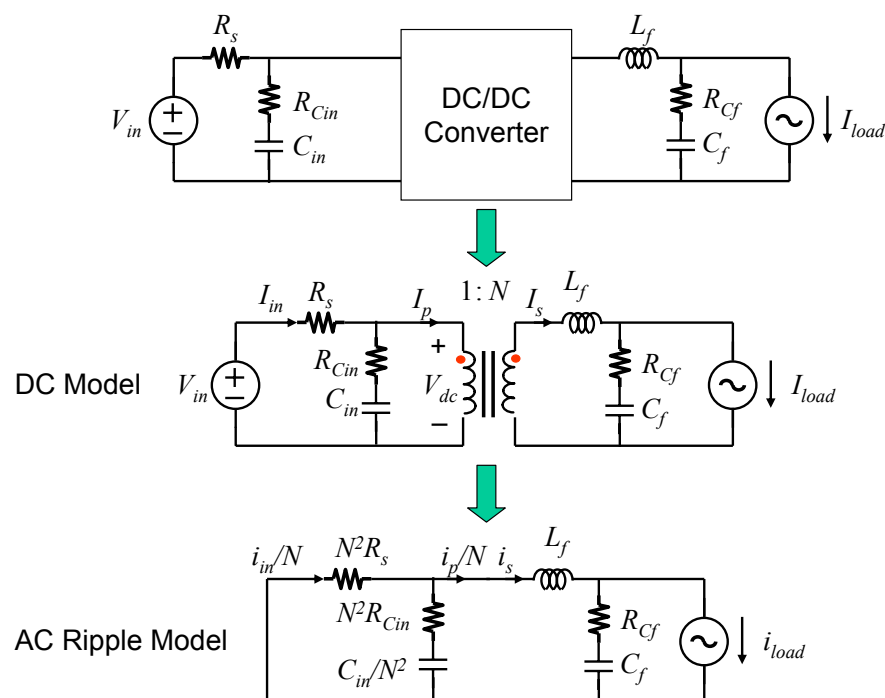

124

Solutions to Ripple Currents

- Add more capacitors (ultra capacitor) on the low-side dc bus
- Add more capacitors on the high-side dc bus
- Add one more stage DC-DC converter
- Add an active ripple cancellation circuit
 - with a bidirectional DC-DC converter to stabilize the high-side dc bus voltage
 - with a built-in control function in the DC-DC converter



125


Benchmark DC/DC Converter Parameters for Ripple Study

- Input Voltage: 25V
- Output Voltage: 200V
- Input DC Capacitor: 6mF
- Output DC Capacitor: 2200mF
- Filter Inductor: 84mH
- Inverter Modulation Index: 0.86
- Inverter Load Resistor: 16.7 Ω




126

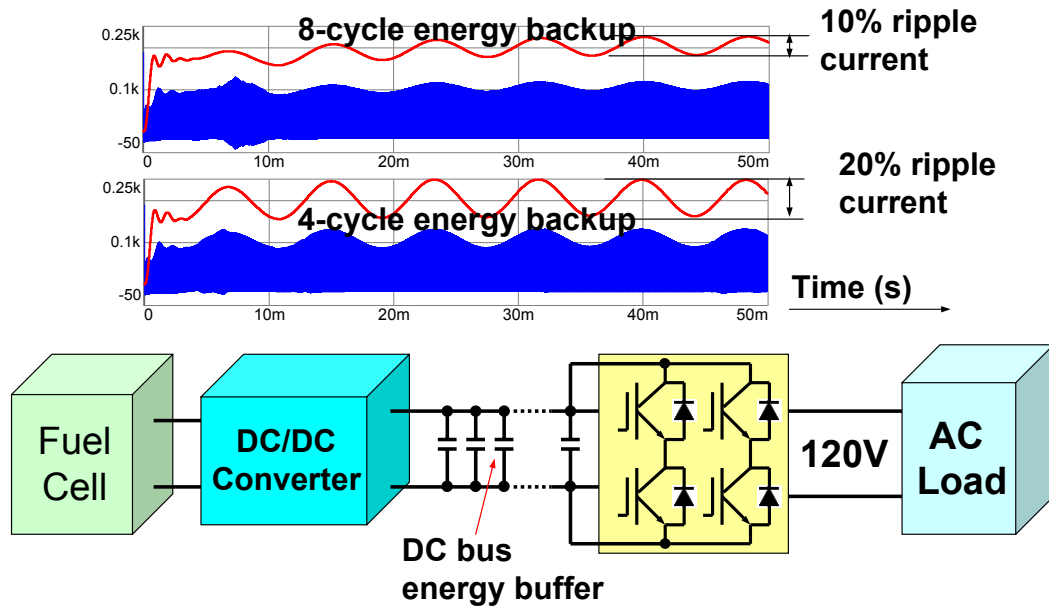Adding Hide-Side Energy Storages on DC Bus Helps Reduce Ripple Current



127

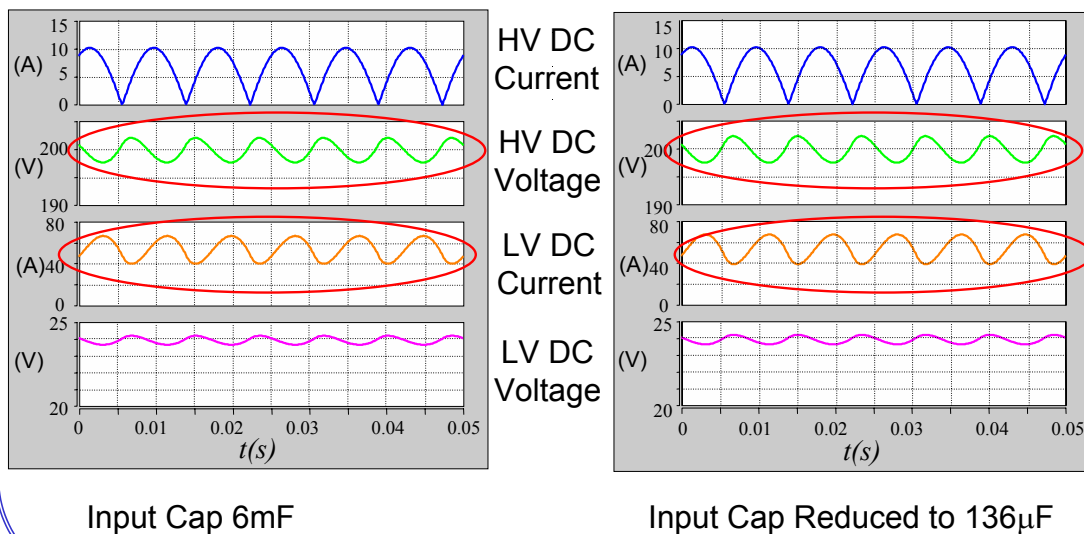
Simulation Results with LV-Side Capacitor Input Capacitor has Very Little Effect to Current Ripple Reduction



128


Output Capacitor can be Used as Passive Solution to Current Ripple Reduction

– Cost is a Concern

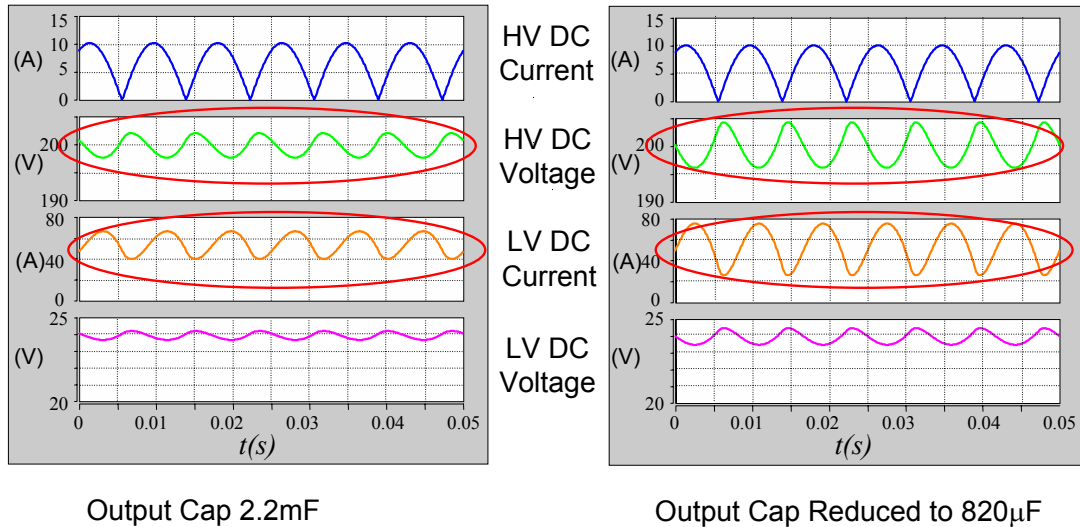

129

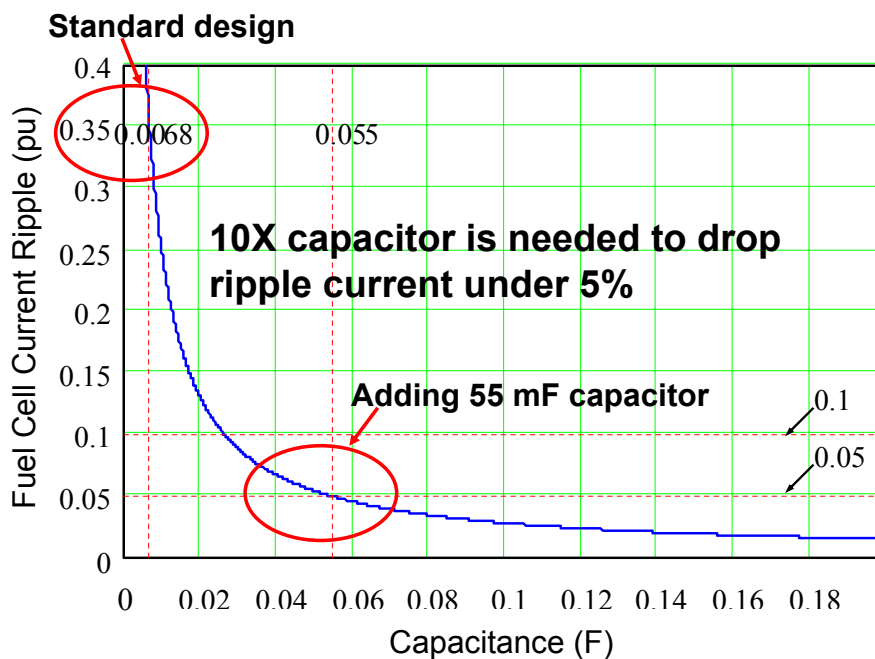Current Ripple Reduction with High-Side Energy Storage Capacitor



130


Features of High-Voltage DC Bus Energy Storage Capacitors

- Fuel cell voltage is low, typically from 36 to 60 V.
- High voltage dc bus voltage is split into two 200 V.
- For a single-phase dual ac outputs such as 120/240 V in US residential systems, the transformer secondary and dc bus can be split in two halves. Each phase leg of the full-bridge along with the split-capacitors becomes a half-bridge inverter to supply 120 V ac output. Summing two 120 V outputs becomes 240 V.
- Multiple capacitors are paralleled for the high-voltage dc bus to store more energy and to provide more transient handling capability during dynamic load change conditions. Energy storage is proportional to CV^2 .
- Size and weight are dominated by passive components. With split DC buses, the volume of energy storage capacitors becomes an issue.

252

131

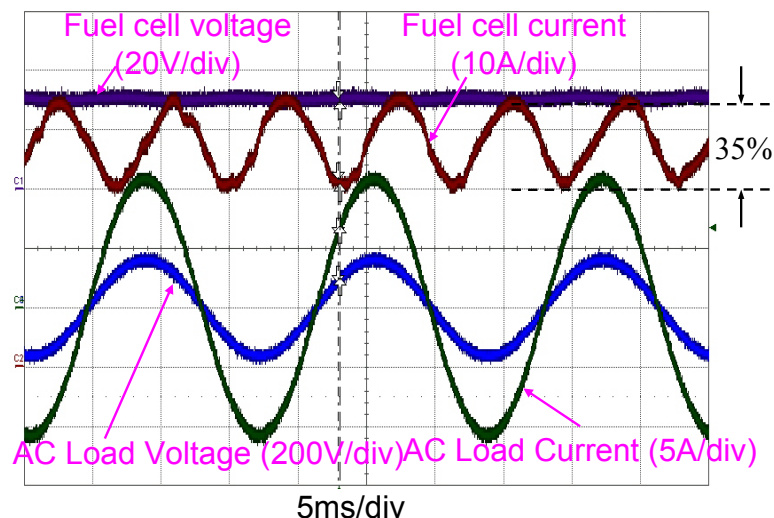Experimental Current Ripples without Adding Capacitors or Controls



252

More than 35% ripple current at the input


132

Fuel Cell Ripple Current Problem is Severe During Load Transients

- For single-phase ac loads, 120 Hz (twice the fundamental frequency) current ripple can reflect back to fuel cell.
- During load transients such as turning on light bulbs or starting up motors, the transient initial current is typically more than 5 times the steady-state current, and the fuel cell ripple current exceeds more 100% or even 200% in some cases.

133

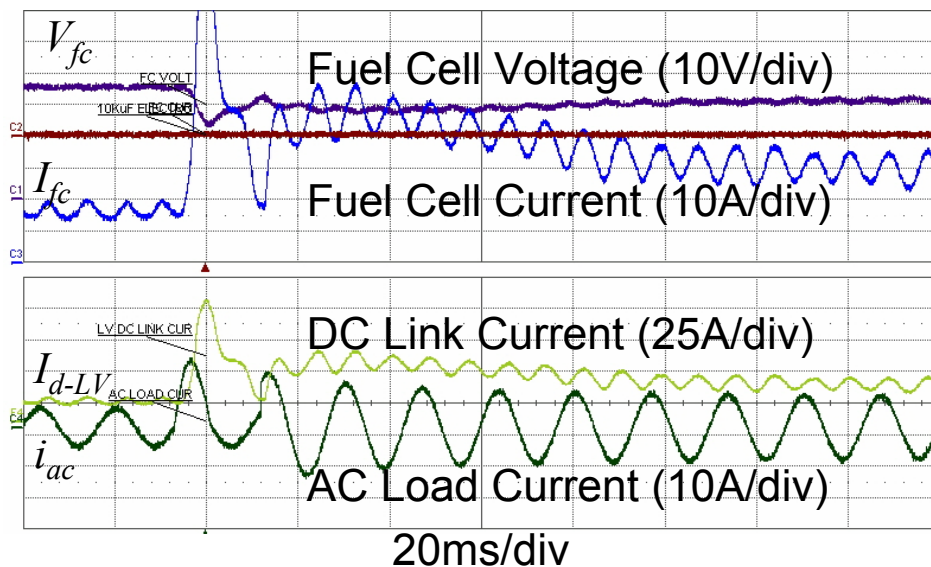
Fuel Cell Responds to AC Load Steps (without Externally Added Capacitor)



Fuel cell sees severe current transient (spike) and current ripple in steady state (35%)

134

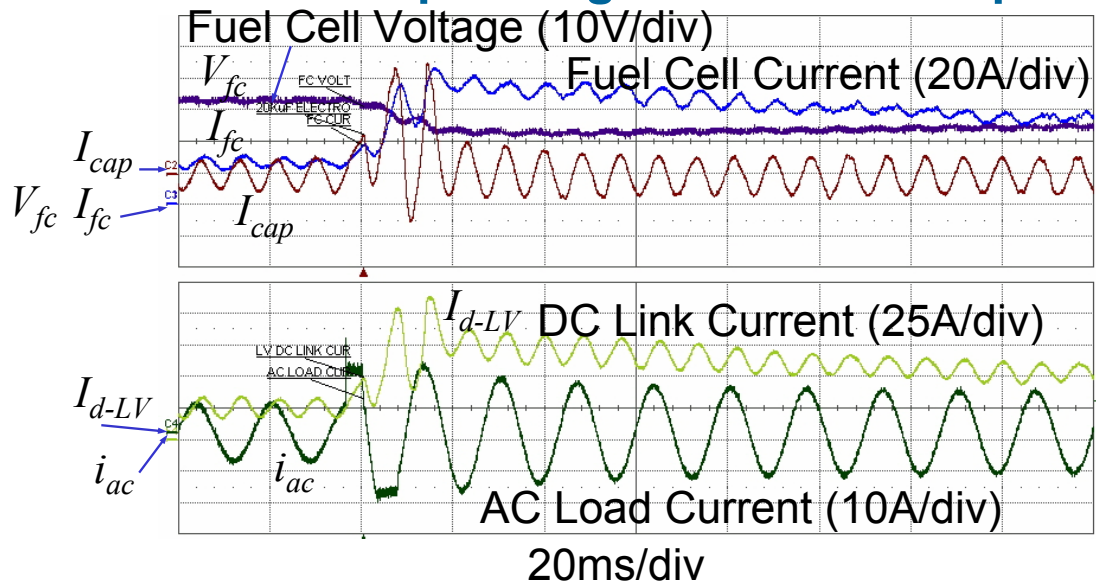Using Electrolytic Capacitor to Smooth Fuel Cell Responding to AC Load Steps




With 20 mF capacitor, fuel cell **current transient** is reduced, but the **current ripple** remains

135


AC Load Transient Response for Fuel Cell with 53-mF Added Capacitors

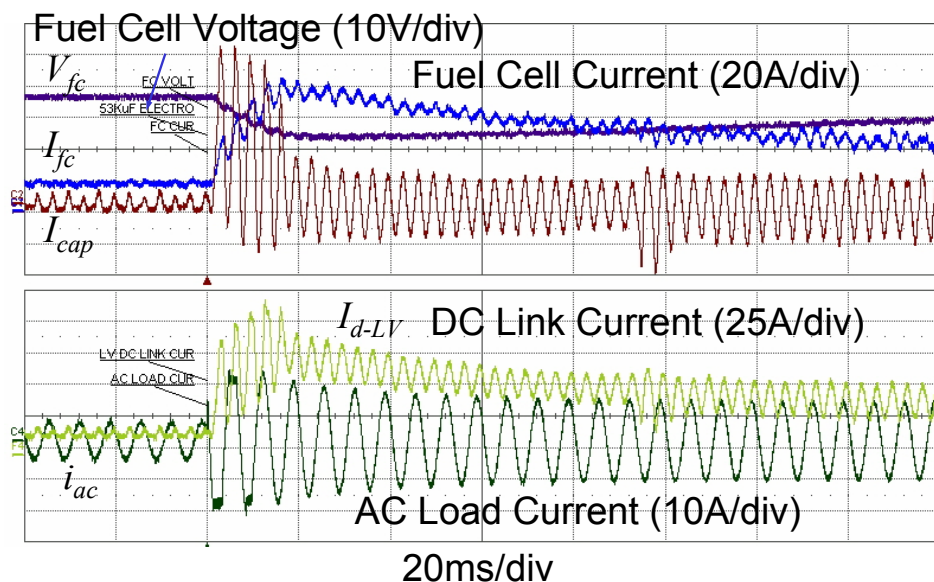Fuel Cell Current Ripple is 5% plus Overshoot




136

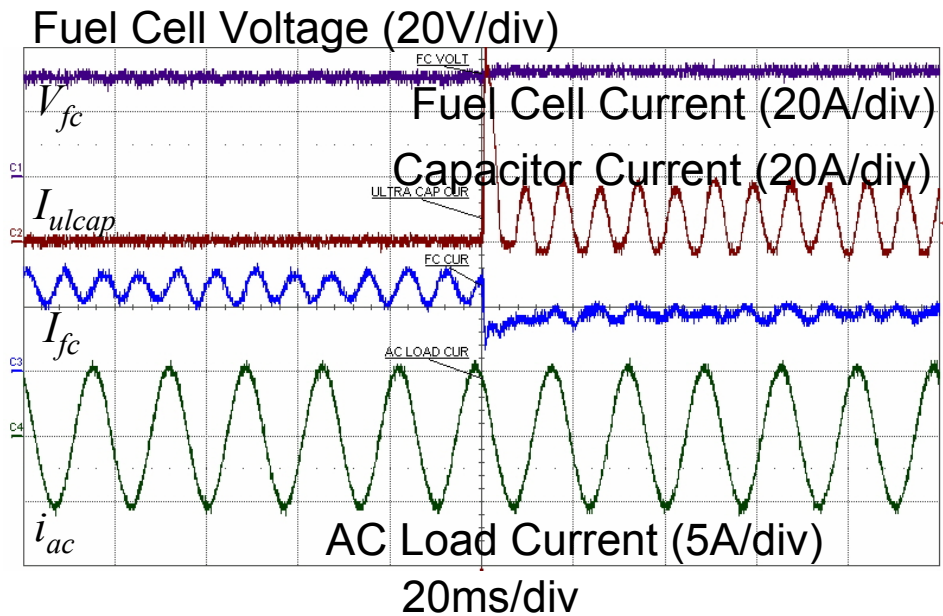Fuel Cell Output Response with an Ultra Capacitor Cut-in




137

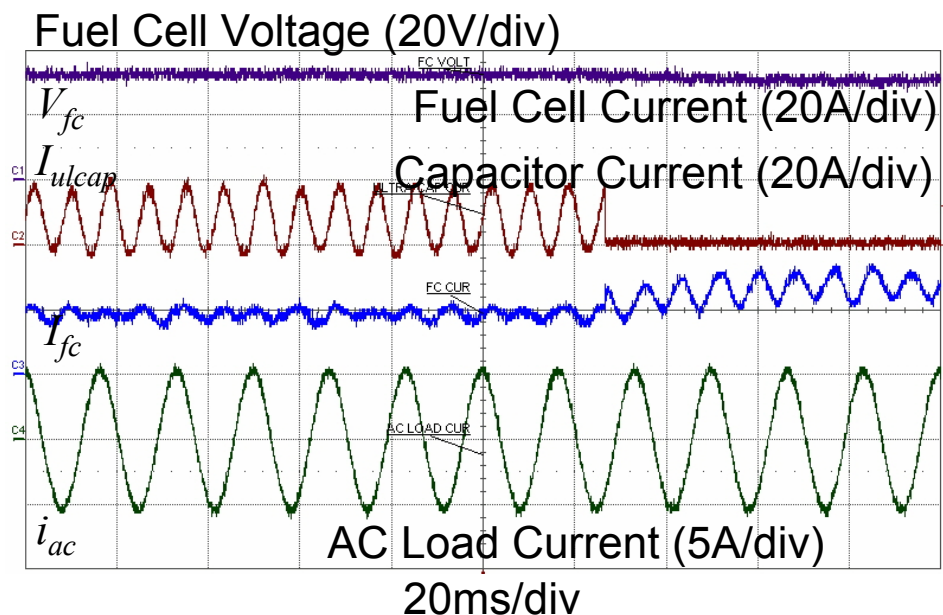Fuel Cell Output Response with an Ultra Capacitor Dropout



138

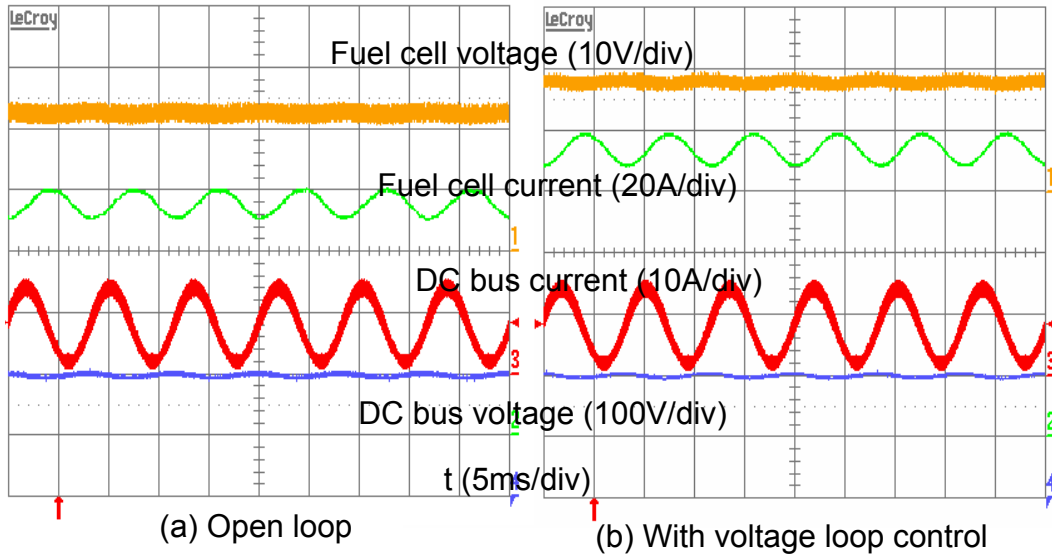
Experiment with Open-Loop and with only Voltage Loop Control



No improvement on current ripple reduction with voltage loop control

139

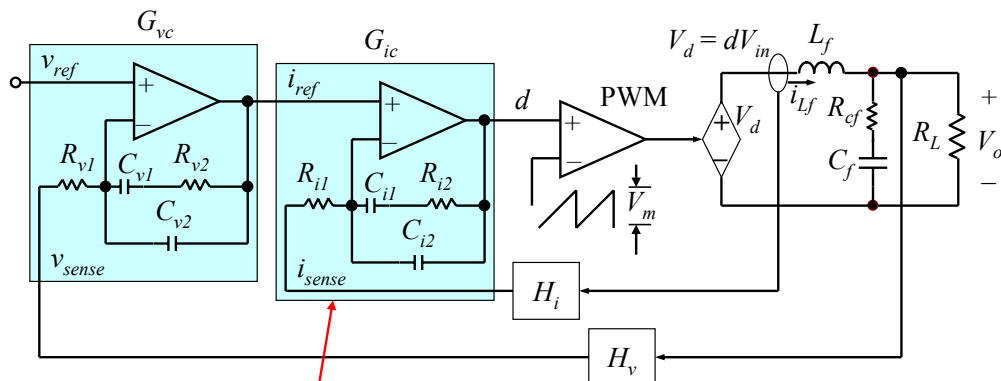Solving Current Ripple with Added Current Loop inside the Voltage Loop




Adding a current loop to regulate the output current

140

Fuel Cell Current Ripple Reduction with the Proposed Active Control Technique

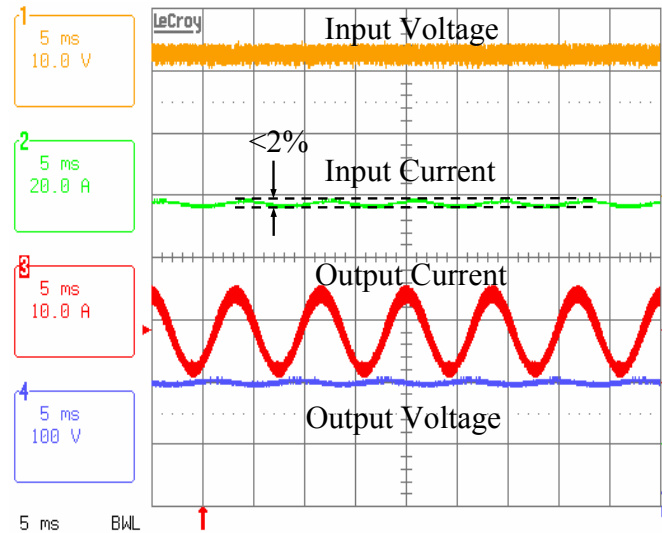Fuel Cell Current Ripple is Reduced to 2%



141

Summary of V6 DC-DC Converter with Active Ripple Cancellation

- High efficiency with a wide-range soft switching: **97%**
- Cost reduction by cutting down passive components
 - Output inductor filter reduction with three-phase interleaved control: **6X**
 - Input high frequency capacitor reduction: **6X**
 - Output capacitor reduction with active ripple reduction: **10X**
- Reliability enhancement
 - No devices in parallel
 - Soft-start control to limit output voltage overshoot
 - Current loop control to limit fuel cell inrush currents
- Significance to SOFC design
 - Stack size reduction by efficient power conversion and ripple reduction: **20%**
 - Inrush current reduction for reliability enhancement

142

10. Recap

1. Basic DC-DC converters and DC-AC inverters are introduced
2. Circuit topology selection can be misled by schematic diagram. Some important considerations are
 - Device voltage and current stresses
 - Number of paralleled devices
 - Parasitic components and losses
3. Advanced V6 DC-DC converter not only shows superior performance but also low production cost
4. Fuel cell current ripple issue can now be solved with advanced current control developed by Virginia Tech without adding cost penalty